

Score released: Quiz 1 - 2020012 x Quiz 1 x

docs.google.com/forms/d/e/1FAIpQLScaNVkjsvpU4aYnKyIVHELeURR9CsO-HDFi0qihuYef\_LCJLg/viewscore?sid=4a4f8f75d7f540d98&vc=0&c=0&w=1&flr=0&token=S6lu-XUBAAA.nTADUAeLISTIKB...

Apps Gmail YouTube Maps Dashboard | Hacker... CALENDER Classroom My Drive - Google... Dashboard Solve IT105/110-La... BECLectures - Goog... PC109 EDW 2020\_Fi... DA -mail box »

✓ What is the wavelength of 50 Hz electrical signal? 1/1

- ☐ 600 Km
- ☒ 6000 Km ✓
- ☐ 6000 m
- ☐ 600 m

✓ When are you operating a cell phone, what kind of circuit are you handling? (Assume that cell phone operates at a frequency 1.9GHz) 1/1

- ☐ Lumped
- ☒ Distributed ✓
- ☐ All of the above
- ☐ None of the above


✓ Find out the resistance R (All resistances are in ohm). 1/1

Type here to search

12:04 07-01-2021 ENG

✓ Find out the resistance R (All resistances are in ohm).

1/1

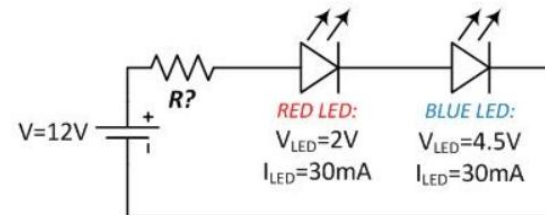


- ☐ 250
- ☐ 200
- ☐ 333.33
- ☒ 183.33



✓ Find out the value of the resistance (in Ohm) from the figure.

1/1

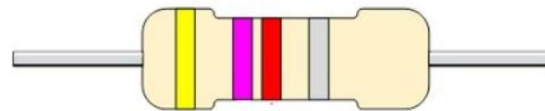

- ☒ 4700



Score released: Quiz 1 - 2020012

Quiz 1

docs.google.com/forms/d/e/1FAIpQLScaNVkjsvpU4aYnKyIVHELeURR9CsO-HDFi0qihuYef\_LCJLg/viewscore?sid=4a4f8f75d7f540d98&vc=0&c=0&w=1&flr=0&token=S6lu-XUBAAA.nTADUAeLISTIKB...

Apps Gmail YouTube Maps Dashboard | Hacker... CALENDER Classroom My Drive - Google... Dashboard Solve IT105/110-La... BECLectures - Goog... PC109 EDW 2020\_Fi... DA -mail box

4700

✓

5000

4.7

5

✗ CRO can be used to

0/1

Do all of the above

Measure the frequency of the signal

✗

Compare the phases and frequencies of signals

Determine the amplitude of the signal

Correct answer

Do all of the above

This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms

Windows Taskbar

Type here to search

Taskbar Icons

System Tray

Score released: Quiz 2 - 2020012 x Quiz 2 x +

docs.google.com/forms/d/e/1FAIpQLSfwOjko-HPjn5ZEnE56rlknC27FzVO-GCI2k5fG867Xo\_II7A/viewscore?sid=7024e4334a970b&vc=0&c=0&w=1&flr=0&token=MzzPCHYBAAA.nTADUAeLISTIKBr... ☆ ⚙ J

Apps Gmail YouTube Maps Dashboard | Hacker... CALENDER Classroom My Drive - Google... Dashboard Solve IT105/110-La... BECLectures - Goog... PC109 EDW 2020\_Fi... DA -mail box »

✓ 1/1

How long can a 12V battery supply 300A to a starter motor if the battery has  $3.6 \times 10^6$  J of chemical energy that can be converted to electric energy?

☒ 1000 seconds ✓

☐ 5000 seconds

☐ 500 seconds

☐ 100 seconds

✓ Check whether the following system is linear.  $y(t) = 2x(t)+3$  1/1

☐ Linear

☒ Non-linear ✓


✓ Find out the expression of the following plot in terms of unit step functions 2/2

4

Type here to search

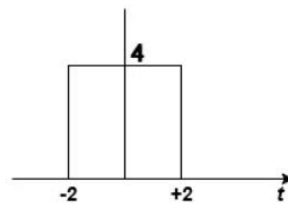
12:05 07-01-2021

✓ Find out the expression of the following plot in terms of unit step functions 2/2



- ☐  $4u(t+2)+4u(t-2)$
- ☐  $4u(t+2)$
- ☐  $4u(t-2)$
- ☒  $4u(t+2)-4u(t-2)$  ✓

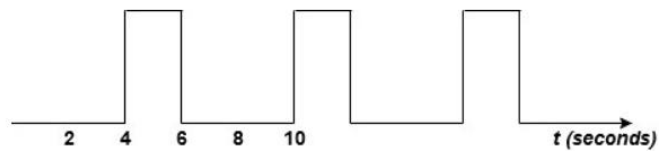✓ Findout the duty cycle of the following square wave. 1/1



- ☐ 75%
- ☐ 50%

☐  $4u(t+2)+4u(t-2)$


☐  $4u(t+2)$

☐  $4u(t-2)$

☒  $4u(t+2)-4u(t-2)$  ✓

✓ Findout the duty cycle of the following square wave.

1/1

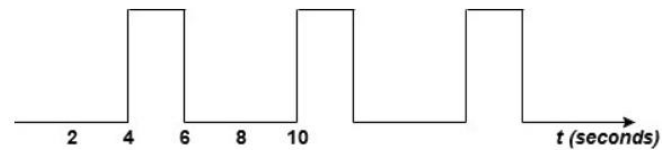

☐ 75%

☐ 50%

☐ 25%

☒ 33% ✓

This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms

Score released: Quiz 3 - 2020012

Quiz 3

docs.google.com/forms/d/e/1FAIpQLScKbQ-cede6YfUJ8Hgab9c5JI5goNNr8ejGOaqnGT0DBUf3w/viewscore?sid=2a6ae8652aaddc69&vc=0&c=0&tw=1&flr=0&token=qrRqHnYBAAA.nTADUAeLIS...

Apps Gmail YouTube Maps Dashboard | Hacker... CALENDER Classroom My Drive - Google... Dashboard Solve IT105/110-La... BECLectures - Goog... PC109 EDW 2020\_Fi... DA -mail box

✓

The electron beam in a TV picture tube carries  $10^{15}$  electrons per second. As a design engineer, determine the voltage needed to accelerate the electron beam to achieve 4 W.

1/1

☒ 25 kV

☐ 25 V


☐ 16 V

☐ 4.6 kV

✓

Find out the expression in terms of unit step function.s

2/2

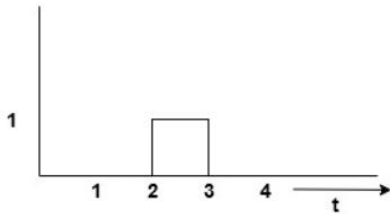

☐  $u(t-2)+0.5u(t-3)$

☐  $0.5u(t-2)-u(t-3)$

☒  $u(t-2)-u(t-3)$

☐  $0.5u(t-2)+0.5u(t-3)$


Windows Taskbar

Type here to search

Taskbar Icons: File Explorer, Google Chrome, WhatsApp, Microsoft Edge, Visual Studio Code

System Tray: Network, Volume, Date/Time (12:06, 07-01-2021), Language (ENG)

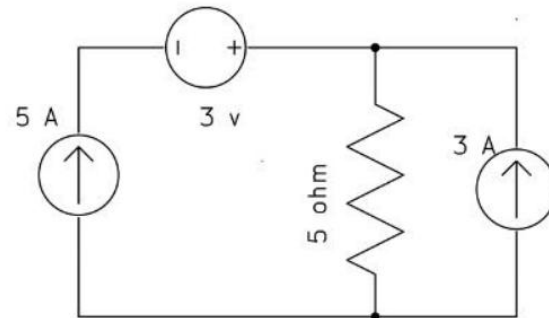
✓ Find out the current that flows through the voltage source. 1/1



- ☐ 8 A
- ☐ 2 A
- ☒ 5 A
- ☐ 3 A




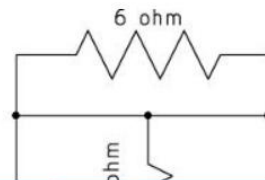✗ Find the voltage across the current source. .../1





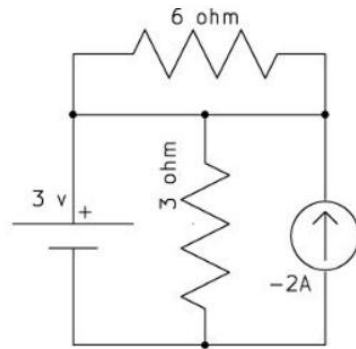✗ Find the voltage across the current source. .../1




2 ✗

Correct answers

- 3 v
- 3v
- 3 V
- 3V
- 3 volts
- 3 volt
- 3 Volts
- 3 Volt
- Three volts
- threevolts

✓ Find the equivalent resistance.

2/2


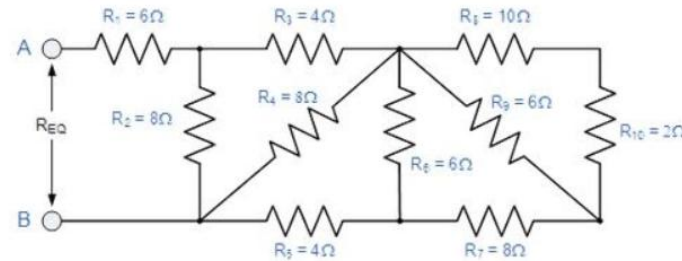


10 ohm

✓

✓ Find the expression of  $x(t)$  (Fig.b) in terms of  $f(t)$  (Fig.a)



2/2

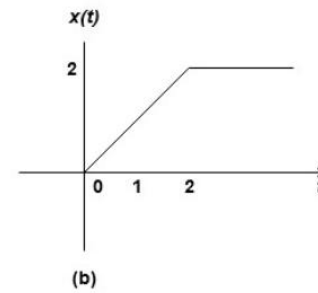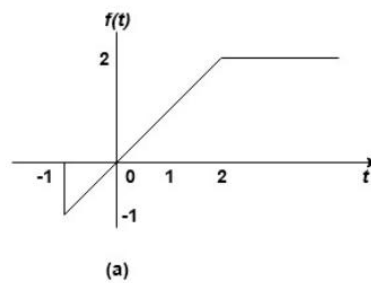

☒  $f(t)u(t)$

✓

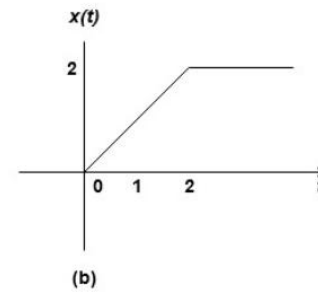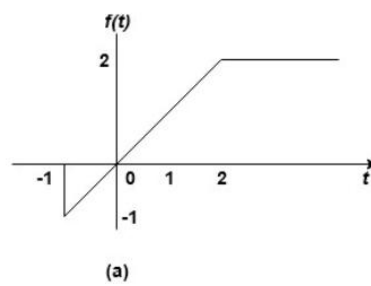✓ Find the expression of  $x(t)$  (Fig.b) in terms of  $f(t)$  (Fig.a) 2/2



- ☒  $f(t)u(t)$
- ☐  $f(t-1)u(t-1)$
- ☐  $f(t-1)u(t)$
- ☐  $f(t)u(t-1)$



✗ Find out the expression of  $f(t)$  in terms of unit ramp function. .../2



☐  $f(t-1)u(t)$

☐  $f(t)u(t-1)$

✗ Find out the expression of  $f(t)$  in terms of unit ramp function. .../2



$4u(t+1)+4u(1-t)$  ✗

Correct answers

$$f(t) = 4r(t+1)-8r(t)+4r(t-1)$$

$$4r(t+1)-8r(t)+4r(t-1)$$

This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms

Search results - 202001233@daii x | Score released: Quiz 5 - 2020012 x | Quiz 5 x +

docs.google.com/forms/d/e/1FAIpQLSfhcao7BOUBCcqjR52Cj-hR8vO7JeMGhrmVMAHJqO-1y2RPEw/viewscore?sid=320e244eadf3f481&vc=08&c=08&w=1&flr=08&token=ndhhQXYBAAA.nTADUAeL... ☆ ⚙ J

Apps Gmail YouTube Maps Dashboard | Hacker... CALENDER Classroom My Drive - Google... Dashboard Solve IT105/110-La... BECLectures - Goog... PC109 EDW 2020\_Fi... DA -mail box »

✓ Find the resistance (in Ohm) of an aluminum wire that has a length of 1000m and a diameter of 1.626 mm. Assume the resistivity of the wire at 20-degree Celsius is  $2.83 \times 10^{-8}$  Ohm-m. 1/1

☐  $2.83 \times 10^{-5}$

☐  $1.36 \times 10^3$


☒  $136 \times 10^{-1}$  ✓

☐  $2.83 \times 10^3$

✓ A nonlinear resistor has a voltage-current relation of  $v = 3i^2 + 4$ . What power does it absorb when energized by 61V? 2/2


266 W ✓

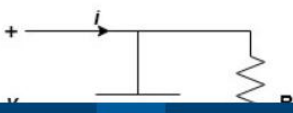✓ The circuit behaves like a filter that filter-out the ripples in the current. For good filtering, the capacitor should able to store energy that is 10 times the energy dissipated by R during 1 cycle. Consider  $R = 10K$ , Ripples has frequency 60 Hz. What is the value of C? 2/2




Windows taskbar: Type here to search, File Explorer, Google Chrome, WhatsApp, A, O, VS Code, System tray: 12:08, 07-01-2021, ENG

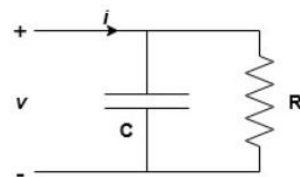✓ The circuit behaves like a filter that filter-out the ripples in the current. 2/2  
For good filtering, the capacitor should able to store energy that is 10 times the energy dissipated by R during 1 cycle. Consider  $R = 10K$ , Ripples has frequency 60 Hz. What is the value of C?



- ☒ 33.3  $\mu F$  ✓
- ☐ 33.3 mF
- ☐ 33 mF
- ☐ 33  $\mu F$

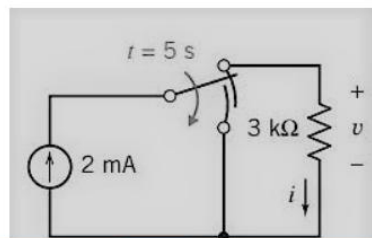
✓ What is the value of the voltage v at time  $t = 6$  s? 1/1



- ☐ 33 mF
- ☐ 33 mF
- ☐ 33 uF

✓ What is the value of the voltage  $v$  at time  $t = 6$  s?

1/1

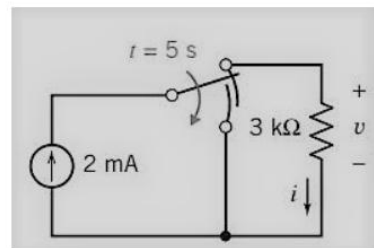

- ☐ 30 V
- ☐ 6 V
- ☒ 0 V
- ☐ 60 V




This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms



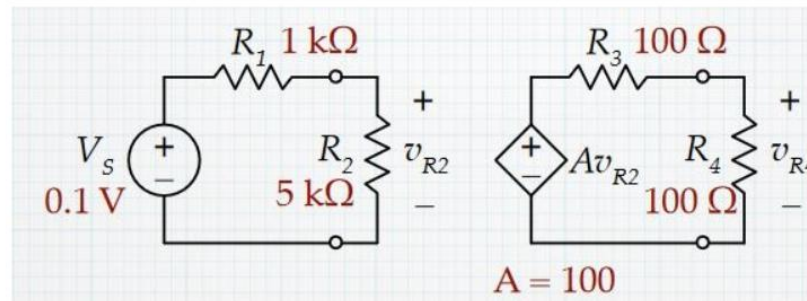✓ Find the voltage  $v_{R4}$  in volt. (No need to write the unit in the answer -- If 3/3 you write it system shall give 0 mark)




4.2 ✗

Correct answer

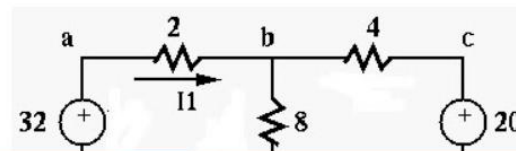4.17

✓ Considering all the units of resistances are in "Ohm", find the current  $I_1$  3/3 (i.e., the current that flows through the ab branch) from the figure below in Amperes. (No need to write the unit in the answer -- If you write it system shall give 0 marks)





$A = 100$


4.2



Correct answer

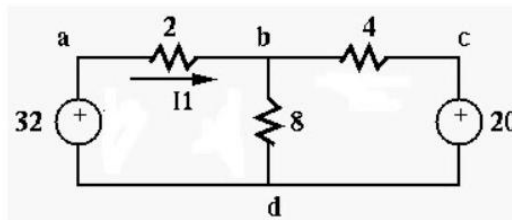4.17

- ✓ Considering all the units of resistances are in "Ohm", find the current  $I_1$  3/3  
(i.e., the current that flows through the ab branch) from the figure below  
in Amperes. (No need to write the unit in the answer -- If you write it  
system shall give 0 marks)



4




This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms

✓ Use Thevenin's theorem to find  $I_o$ .

3/3

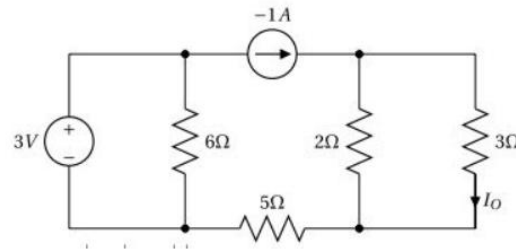


- ☐ -0.33A
- ☐ 0.33 A
- ☐ 0.4 A
- ☒ -0.4 A



✗ Find the equivalent resistance (in Ohm) across AC.

0/3

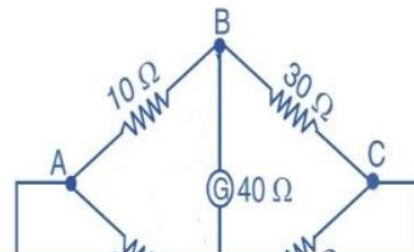


Type here to search



12:09  
07-01-2021

✗ Find the equivalent resistance (in Ohm) across AC.

0/3

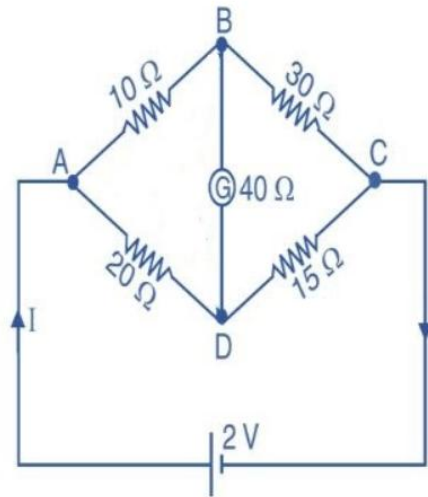

☐ 18.04

☒ 18.67



☐ 35

☐ 40

Correct answer

☒ 18.04




Type here to search



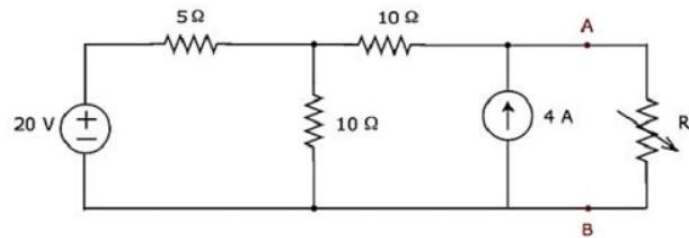12:09  
07-01-2021

✗ Find the maximum power that can be delivered to the load resistor  $R_L$  of 0/2 the circuit.



☒ 40 W

☐  $40/3$  W

☐  $250/3$  W


☐ 200 W

Correct answer

☒  $250/3$  W

✓ Find out the current that flows through the 20 Ohm resistor

2/2

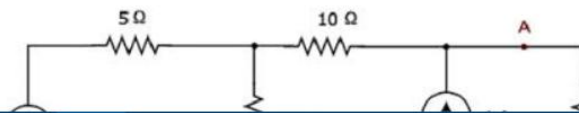

Type here to search




12:09

ENG

07-01-2021

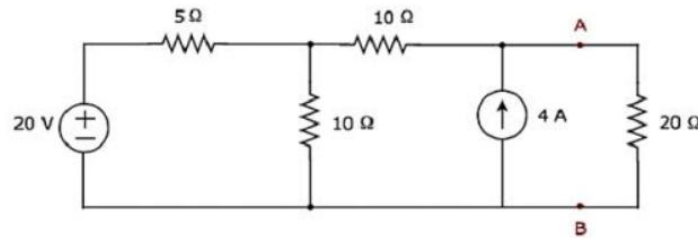
✓ Find out the current that flows through the 20 Ohm resistor 2/2



- ☐ 1 A
- ☐ 4 A
- ☐ 3 A
- ☒ 2 A



✓ Find  $V_0$ . 2/2

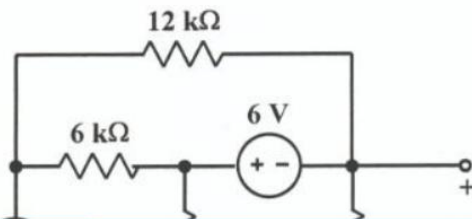


Type here to search



✓ Find  $V_o$ .

2/2

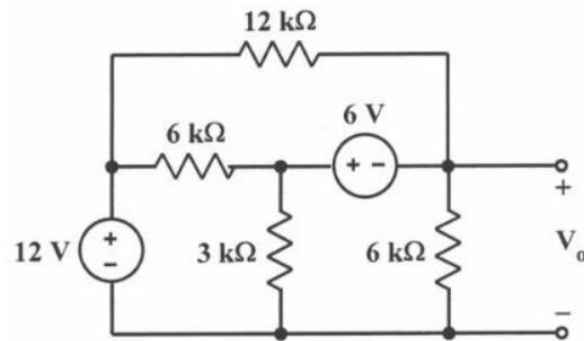

- ☐ 6 V
- ☒ 0 V
- ☐ 3 V
- ☐ 2 V



This form was created inside of Dhirubhai Ambani Institute of Information and Communication Technology.

Google Forms