

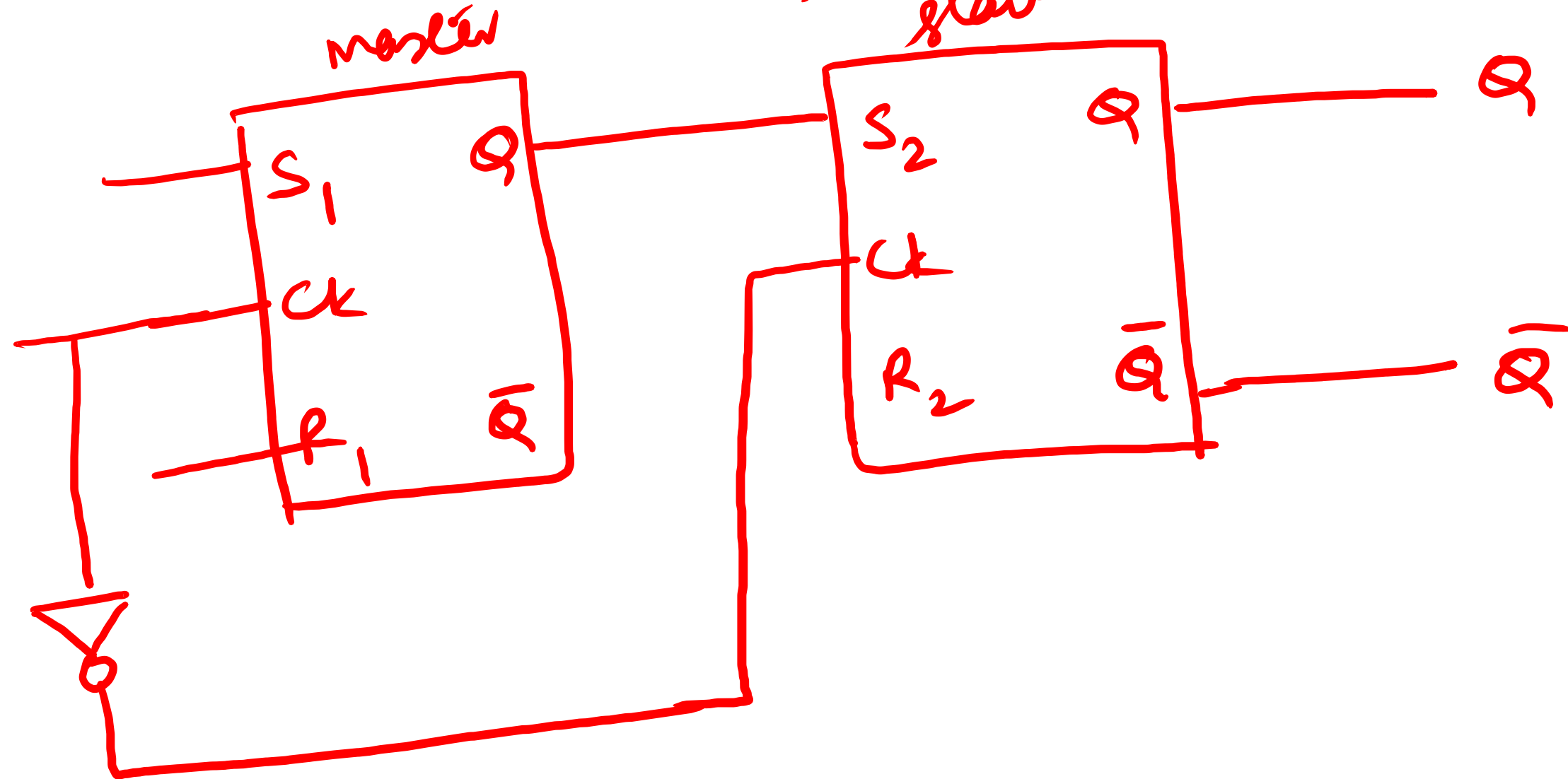


# Master slave ffs

SR master slave ff

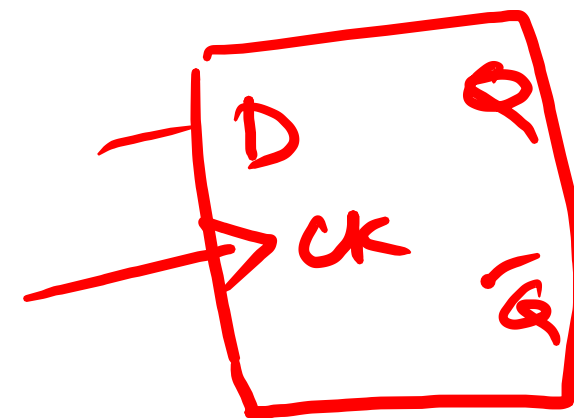


# D master slave ff

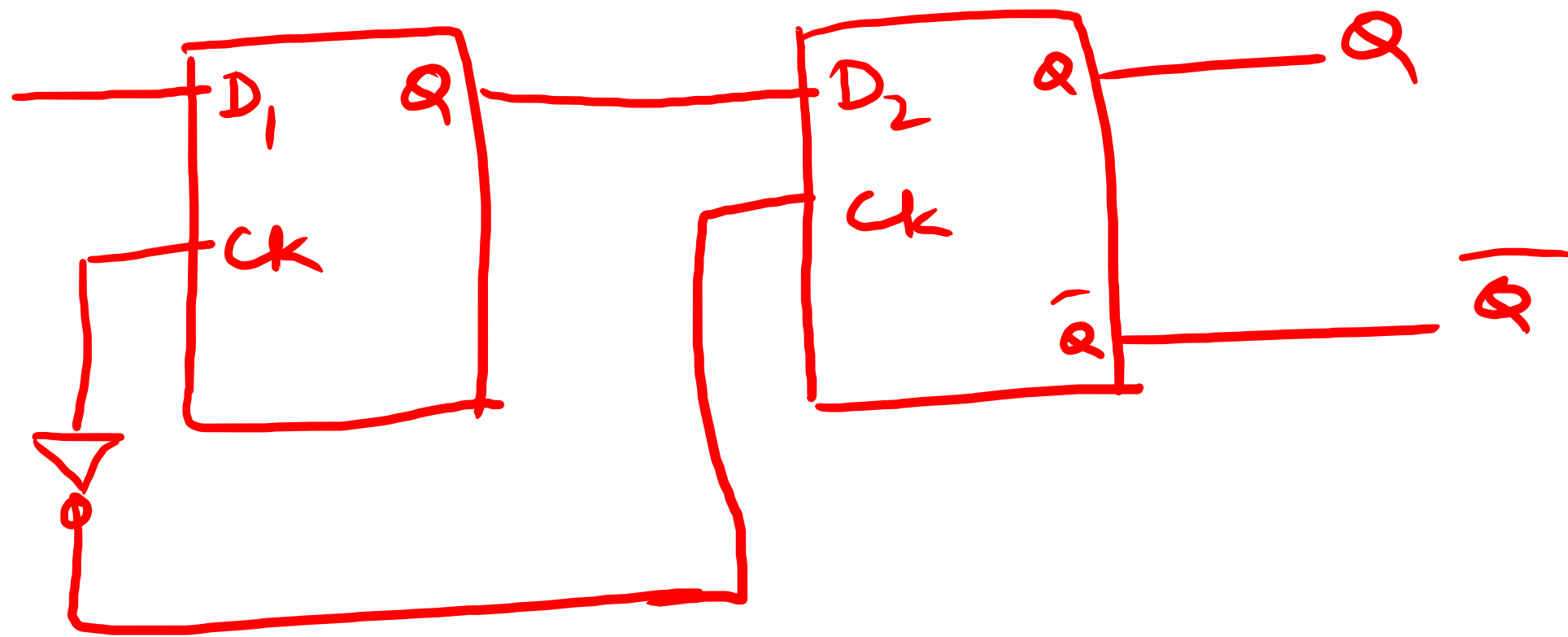

D ff
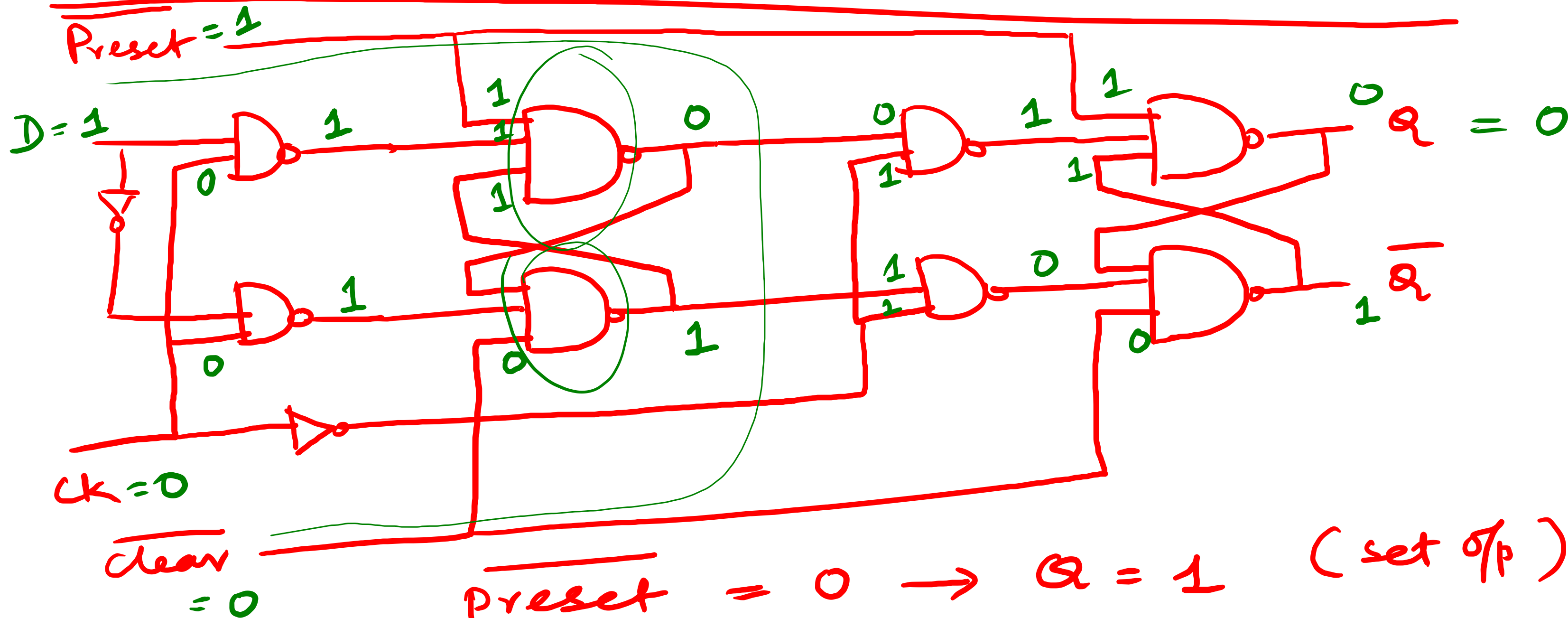
# MS Dff with asynchronous preset & clear



$\overline{preset} = 0 \rightarrow Q = 1$  (set  $Q_p$ )

$\overline{clear} = 0 \rightarrow \underline{Q = 0}$  (reset  $Q_p$ )

# State table of Master Slave D ff with preset & clear


<u>Preset</u>	<u>Clear</u>	<u>Ck</u>	<u>D</u>	<u>Q</u>	<u><math>\bar{Q}</math></u>
0	1	x	x	1	0
1	0	x	x	0	1
0	0	x	x	1	1
1	1	↑	0	0	1
1	1	↑	1	1	0

(not allowed)
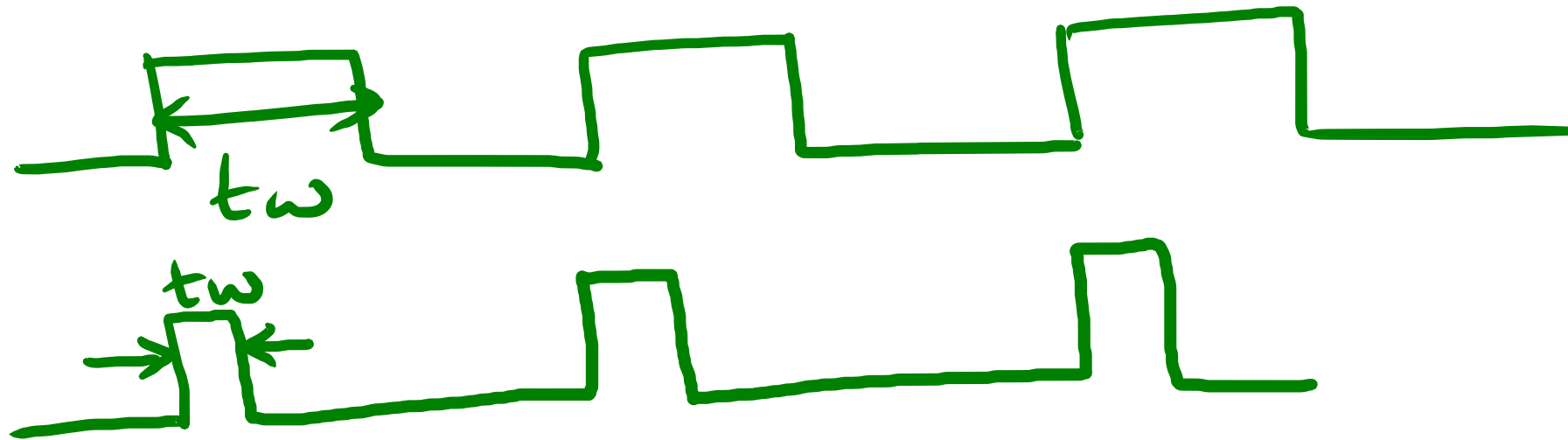
## Timing Issues.

- clock width ( $t_w$ )

Min time for which clock pulse should be high for the flipflops that it feeds to work properly




- Set up time ( $t_{\text{setup}}$ )

Amount of time the i/p to a ff should be stable before the arrival of active edge of clock pulse

- Hold time ( $t_{\text{hold}}$ )

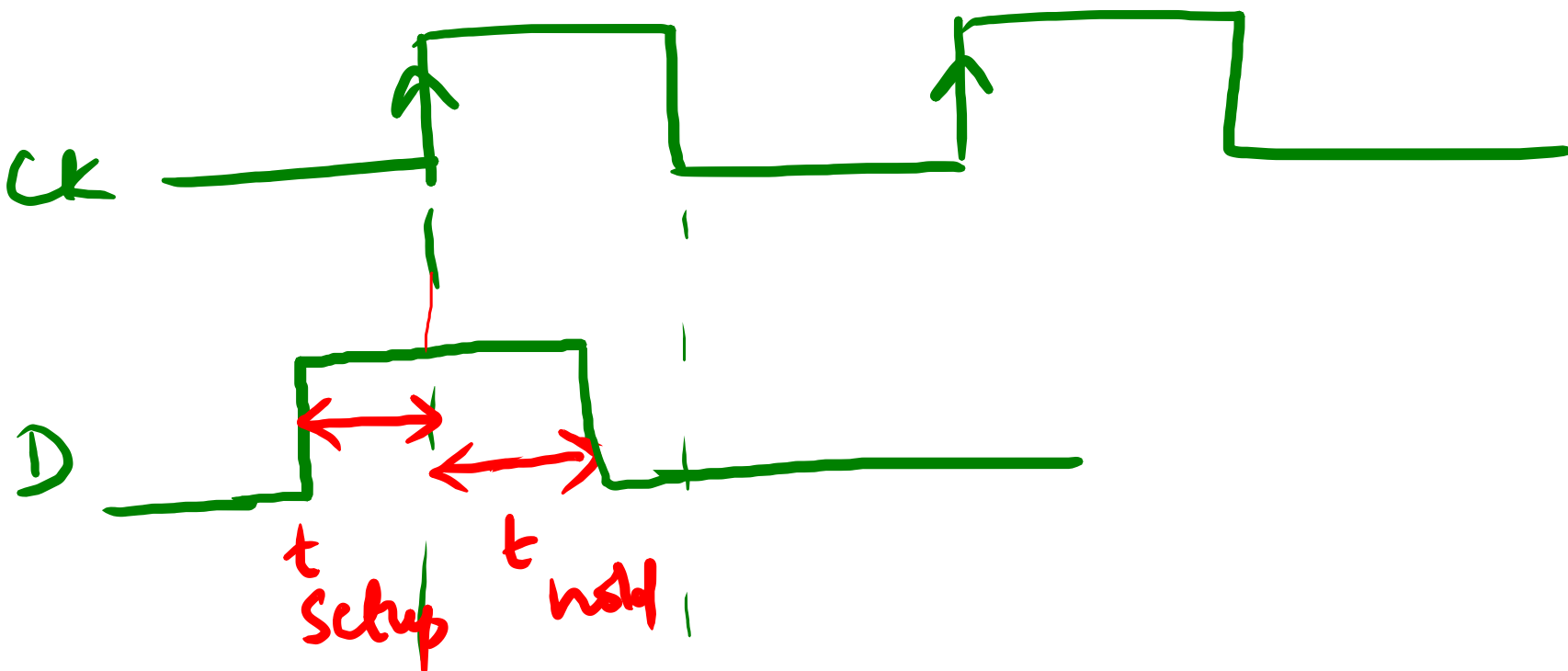Amount of time the i/p to a ff should be stable after the active clock edge arrives.




Propagation delay



$t_{pL-h}$

$t_{p h-l}$

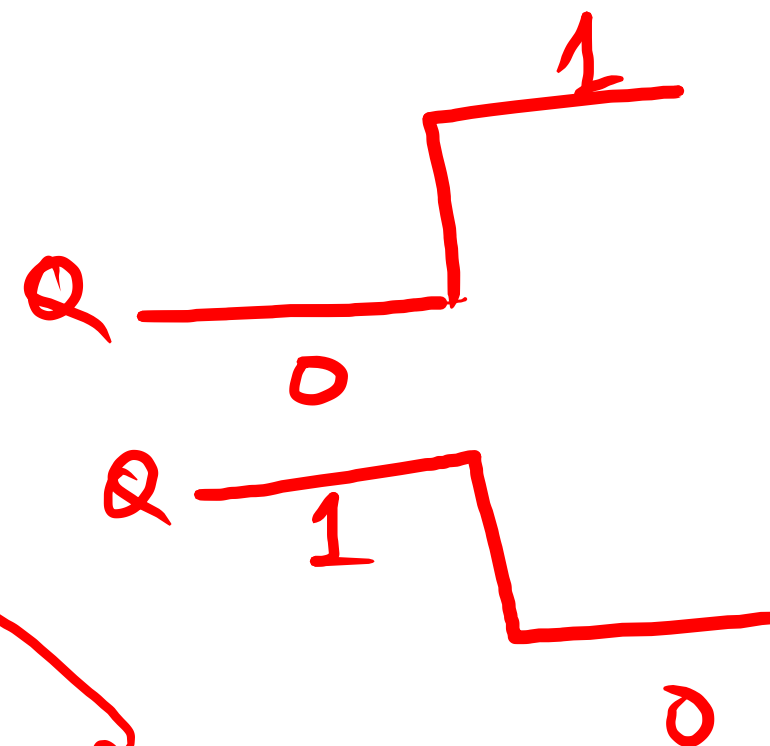

- Various types of ffs / latches.
- clocking
- State table / State diagrams
- Conversion of ff to another

## Design of synchronous sequential cks

1. Derive the state table & state diagram from the problem definition
2. Obtain the minimized form for ff i/ps & o/ps using K map ✓
3. Draw the logic diagrams



Design a synchronous sequential circuit using the D ffs for the state diagram given below

$D_x$

	00	01	11	10
0			1	1
1		1		

$$D_x = \bar{x}y + x\bar{y}A$$

$D_y$

	00	01	11	10
0		1		1
1		1		1

$$D_y = \bar{y}A + y\bar{A} = y \oplus A$$

$Z$

	00	01	11	10
0	1			1
1	1	1	1	1

$$Z = x + \bar{y}\bar{A}$$


State table

PS x y $Q_t$	I/P A	NS $x^+ y^+$ $Q_{t+1}$	FF i/p s $D_x D_y$		o/p Z
00	0	00	0	0	1
00	1	01	0	1	0
01	0	11	1	1	0
01	1	10	1	0	0
10	0	00	0	0	1
10	1	11	1	1	1
11	0	01	0	1	1
11	1	00	0	0	1


$$D_a = \overline{X}Y + X\overline{Y}A$$

$$D_y = Y \oplus A$$

$$Z = X + \overline{Y}A$$

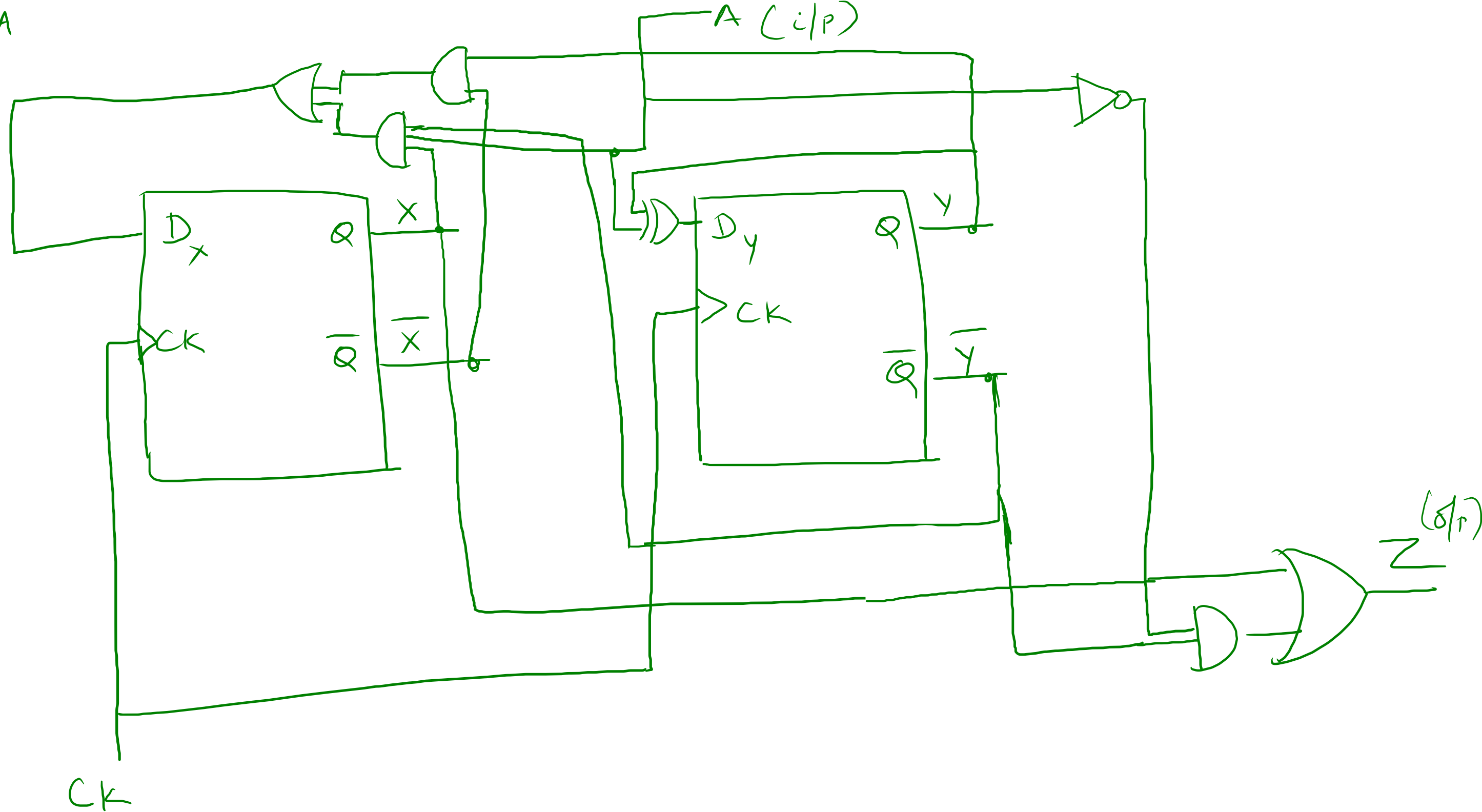

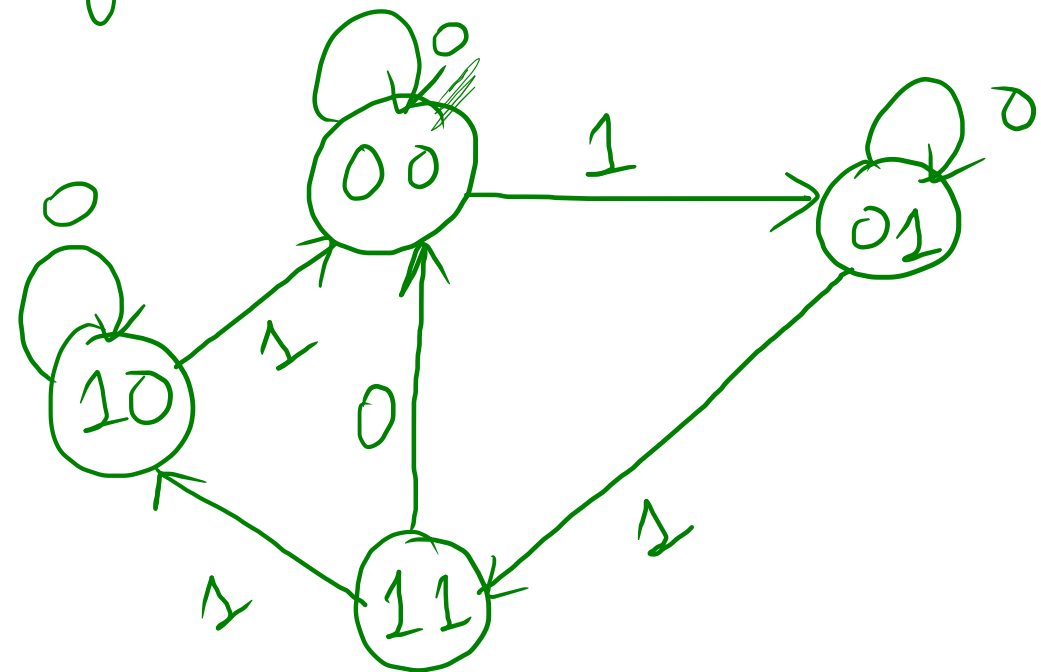Design a synchronous sequential ckt for the state diagram given below using JK ff.



JK excitation table

$Q_t$	$Q_{t+1}$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

0x  
 ↓  
 00  
 01

PS	I/P	NK	FF i/p							
x y	A	$x^+ y^+$	$J_x K_x$	$J_y K_y$	x	y	A	$x^+ y^+$	$J_x K_x$	$J_y K_y$
00	0	00	0 x	0 x	1	1	0	00	x 1	x 1
00	1	01	0 x	1 x	1	1	1	10	x 0	x 1
01	0	01	0 x	x 0						
01	1	11	1 x	x 0						
10	0	10	x 0	0 x						
10	1	00	x 0	0 x						

$J_x$

$x \backslash yA$	00	01	11	10
0			1	
1	x	x	x	x

$J_x = yA$

$x \backslash yA$	00	01	11	10
0	x	x	x	x
1		1		1

$K_x = \bar{y}A + y\bar{A}$   
 $= y \oplus A$

$x \backslash yA$	00	01	11	10
0		1	x	x
1			x	x

$J_y = \bar{x}A$

$x \backslash yA$	00	01	11	10
0	x	x		
1	x	x	1	1

$K_y = x$