 


# Programmable Array Logic

- ① Programmable AND array
- ② Fixed OR array

PAL



 
# Sequential circuits




0 1

Memory → how to store bits electronically





store a 0

 

store a 1
  
# Latches and flipflops

Memory elements used to store information.



## Latch

Both 0 & 1  
2 i/p's & 2 O/p's

Bistable  
device  
multivibrator


① SR (Set - Reset)

② D type (Delay)




③ JK

④ Toggle type


Level sensitive

 

   Latch is a pair of cross coupled NOR or NAND gates



 force the o/p to a specific value by applying appropriate i/p's at R & S.



TT for NOR

	A	B	F
X X	0	0	1
	0	1	0
X X	1	0	0
	1	1	0

$S = 1, R = 0, Q = 1, \bar{Q} = 0 \rightarrow$  set o/p to 1  
 $S = 0, R = 0, Q = 1, \bar{Q} = 0 \rightarrow$  no change (store)  
 $S = 0, R = 1, Q = 0, \bar{Q} = 1 \rightarrow$  set o/p to 0  


---

 $S = 0, R = 0, Q = 0, \bar{Q} = 1 \rightarrow$  NC (store)

# Truth table for SR latch


S	R	Q	$\bar{Q}$
0	0	NC	NC
0	1	0	1
1	0	1	0
1	1	invalid	invalid

NAND TT


0	0	1
0	1	1
1	0	1
1	1	0

Case  $\rightarrow$   $S=0, R=1$   
 $\bar{S}=1, \bar{R}=0, Q=0, \bar{Q}=1$

NAND implementation

 



 

$$S = 0, R = 1$$

$$S = 1, R = 1$$

$$\bar{S} = 0, \bar{R} = 0$$

$$Q = 1, \bar{Q} = 1$$

$$\bar{S} = 1, \bar{R} = 1, Q = 0, \bar{Q} = 0$$

$$S = 0, R = 0 \rightarrow \text{store}$$


## Gated SR latch

Enable i/p  $E$

When  $E = 1$ , the latch is active


When  $E = 0$ , the latch is deactivated

& o/p does not change.


 


E	S	R	Q	Q'
0	x	x	NC	NC
1	0	0	NC	NC
1	0	1	0	1
1	1	0	1	0
1	1	1	invalid	invalid

# Adder subtractor using FAs & MUX

 

$S = 1$ , sub  
 $S = 0$ , add

 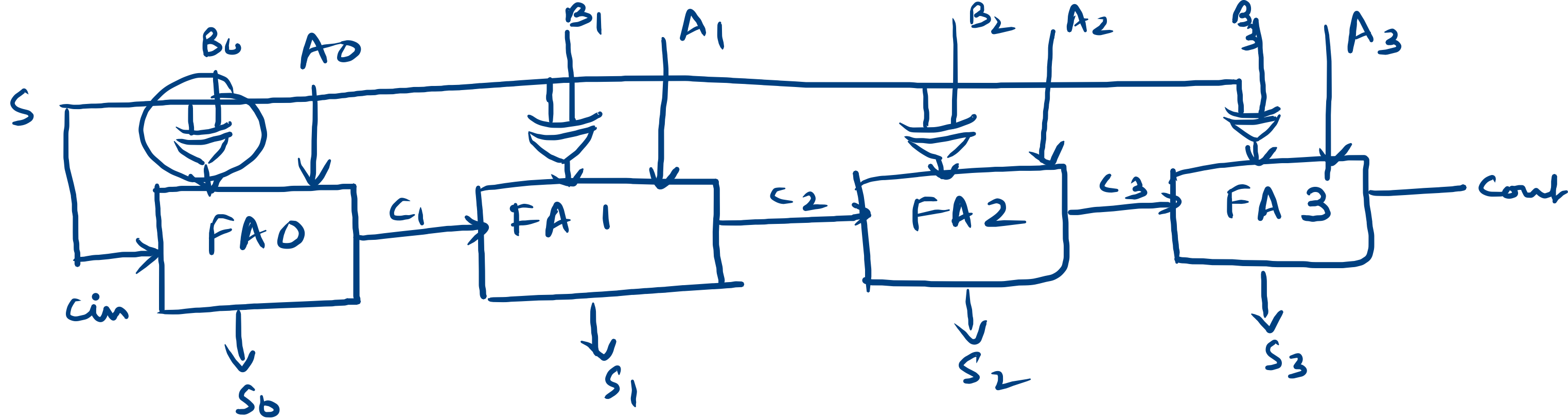

$$S = 0, \quad B_0$$

$$S = 1 \quad - \quad \overline{B_0}$$

Alternate design for SR latch

