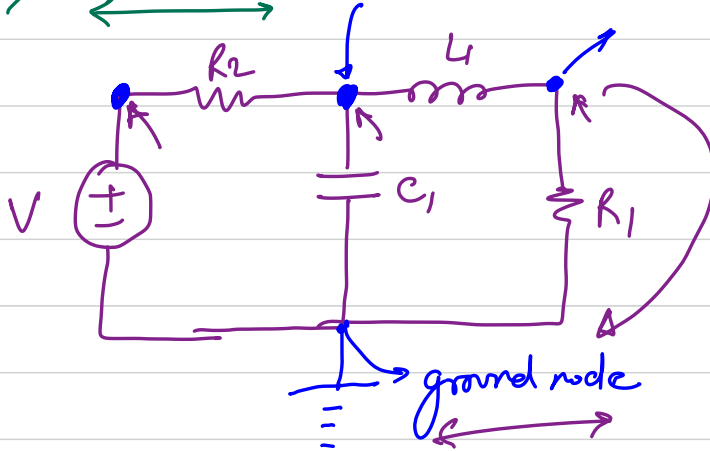



Lecture 5

⊗ Node, Branch




KCL (Kirchhoff's Current law)

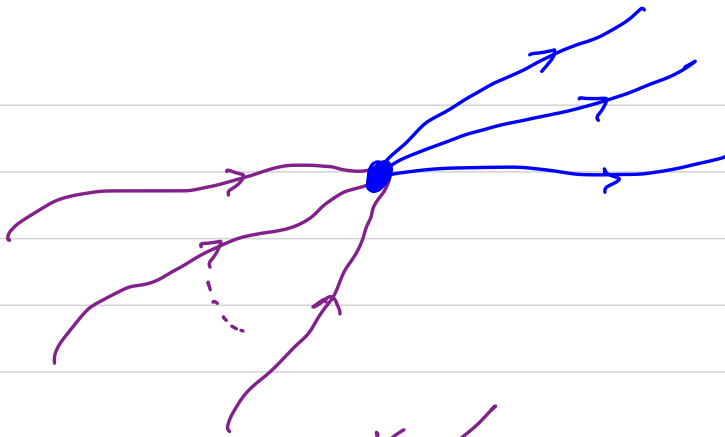
The algebraic sum of currents entering a node = algebraic sum of current leaving the node




$$9\cos 2t = 2\cos 2t + 3\cos 2t + i_R + \cos 2t$$

$$i_R = 3\cos 2t$$

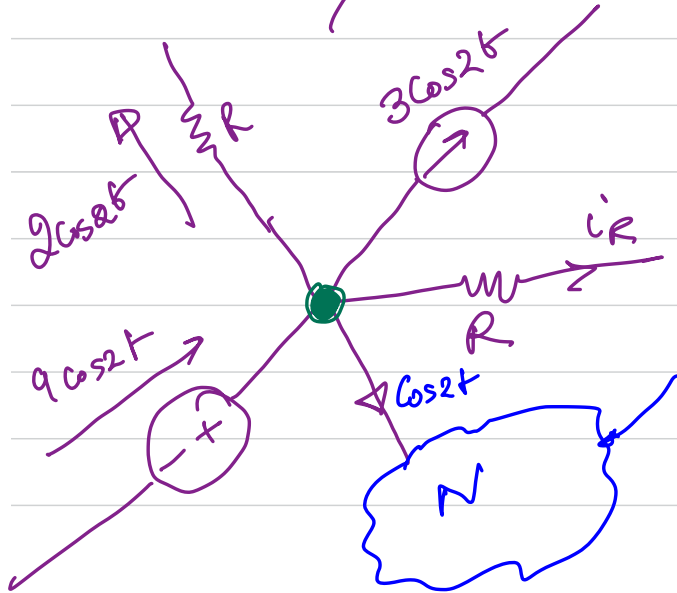

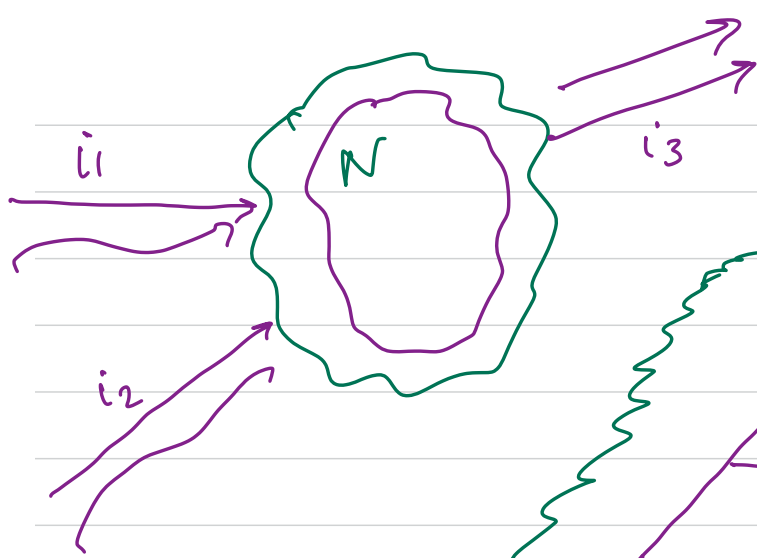


$$i_1 + i_2 = i_3$$

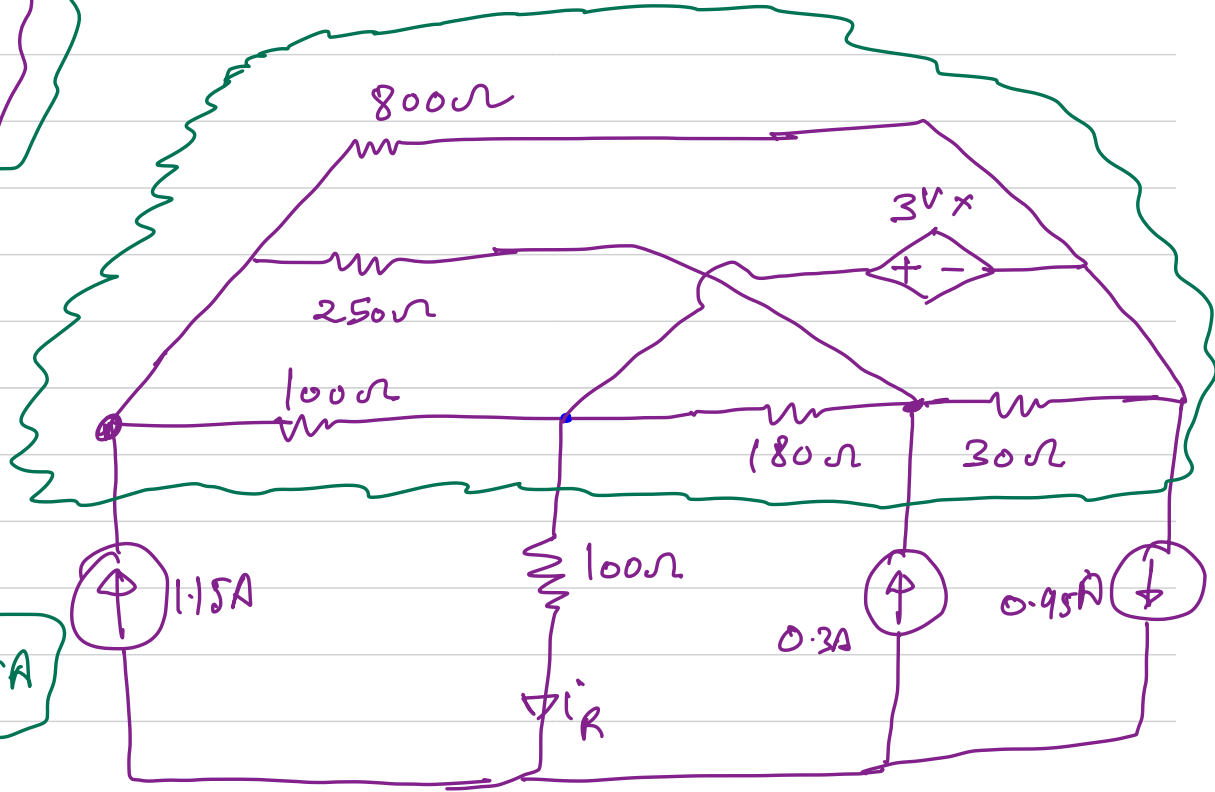

$$1.15 + 0.3A = i_R + 0.95A$$

"KVL"
 \longleftrightarrow

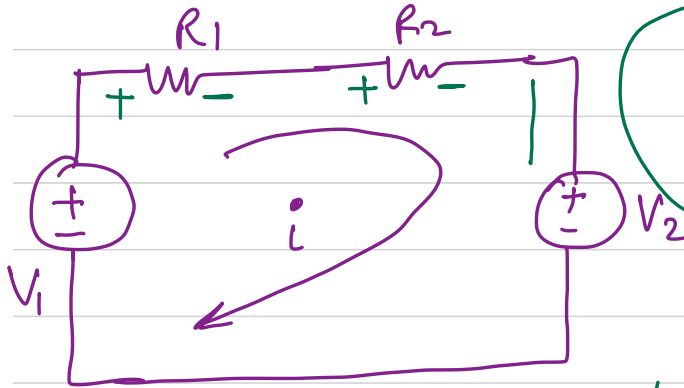
Algebraic sum of voltage drop around any closed path is zero at every instant of time





$$\left\{ +V_1 - iR_1 - iR_2 - V_2 = 0 \right\}$$





$$i = (V_1 - V_2) / (R_1 + R_2)$$
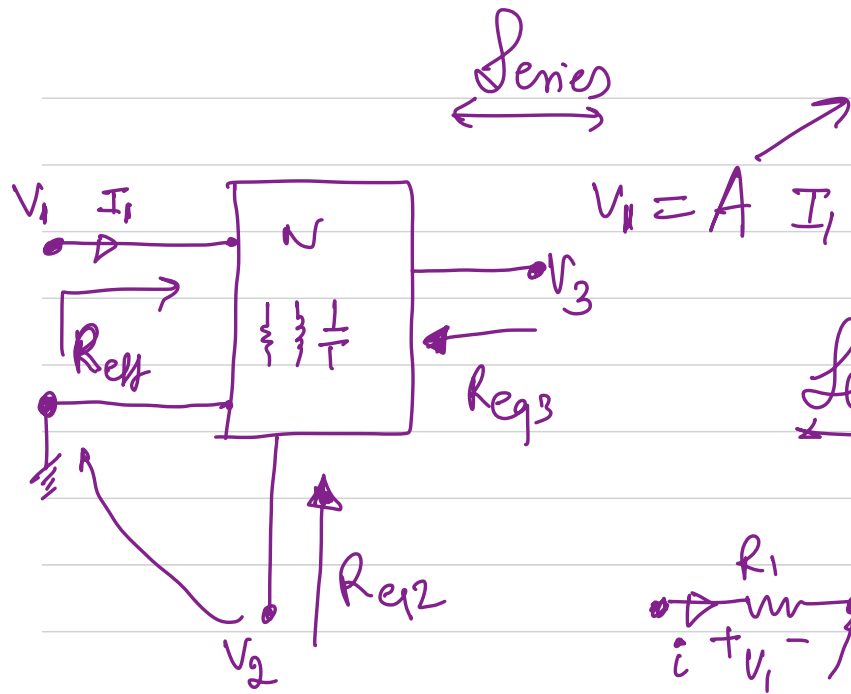
$$\underline{\underline{(-V_1 + iR_1 + iR_2 + V_2) = 0}}$$






Series Connection

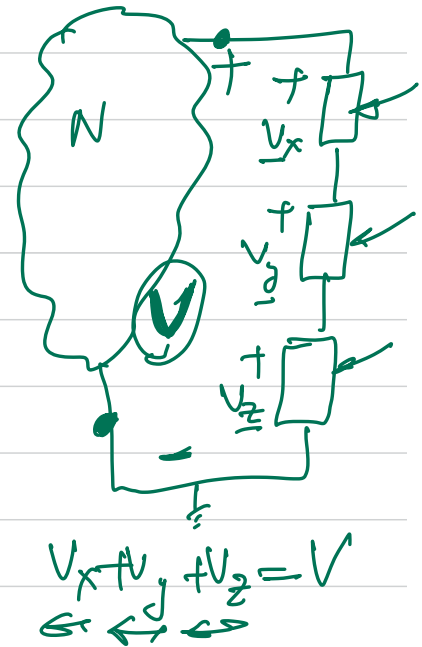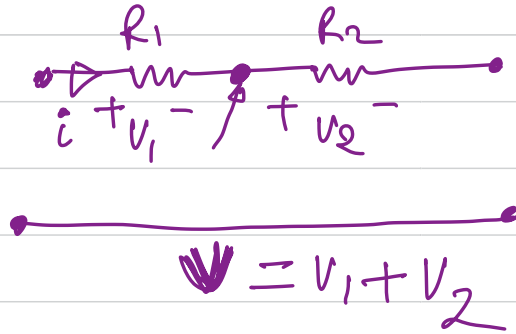

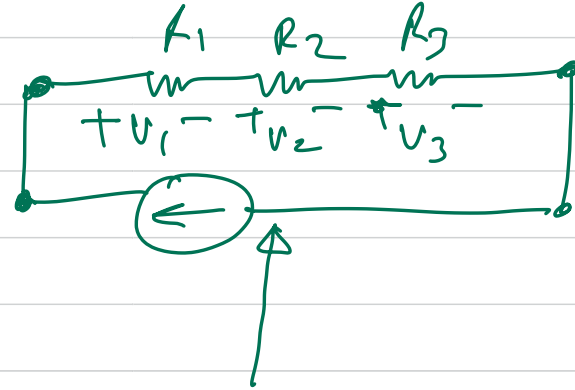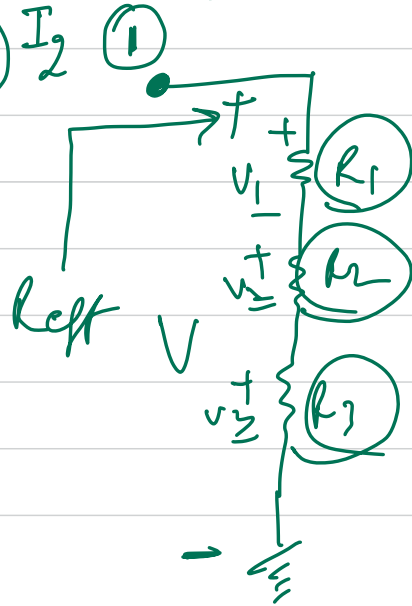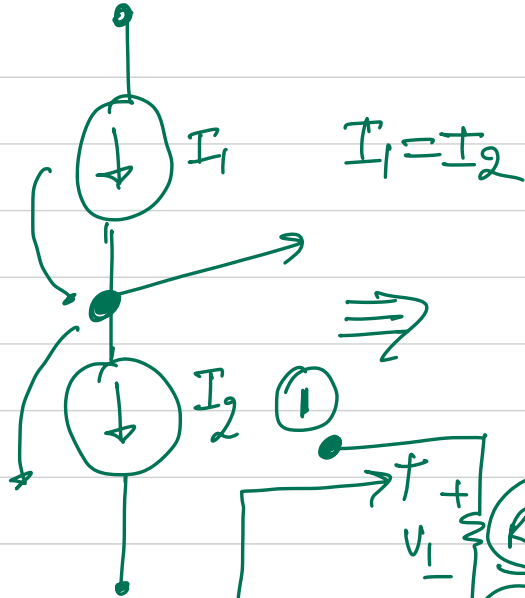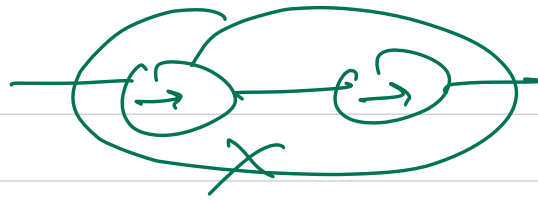

$$R_{eff} = R_1 + R_2 + R_3$$

$$i = \frac{V}{(R_1 + R_2 + R_3)}$$



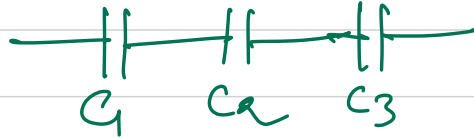
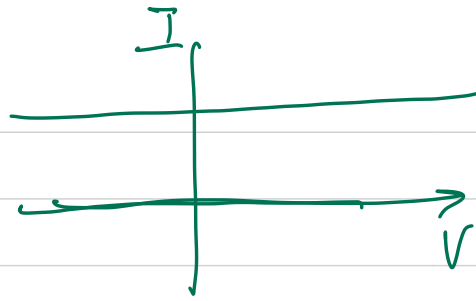
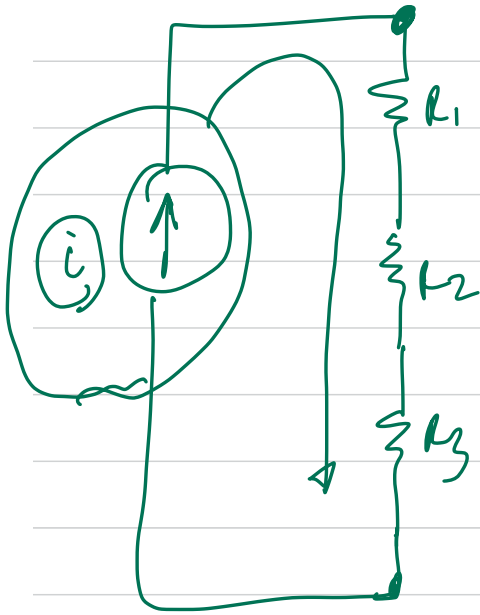


$$\frac{1}{C_{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$


$$V_1 = \frac{1}{C} \int i dt$$





$$L_{eq} = L_1 + L_2 + L_3 \dots$$

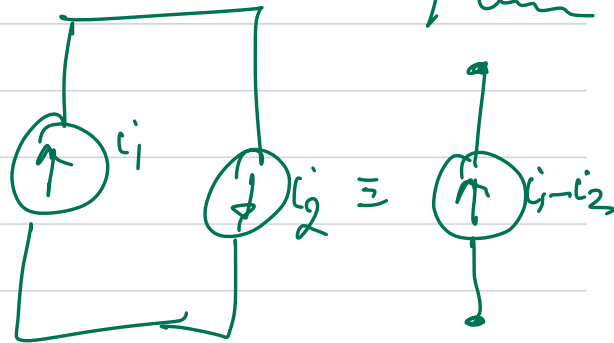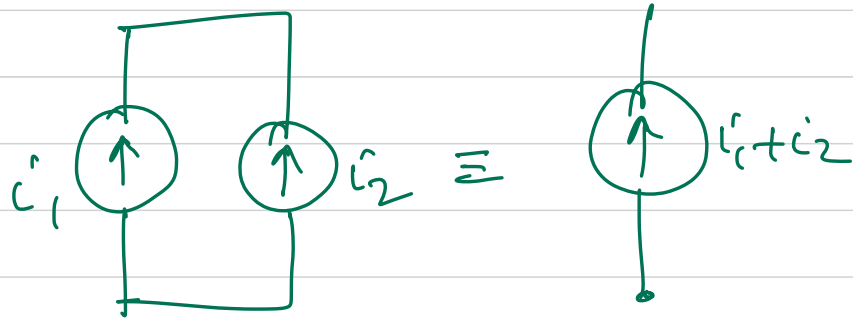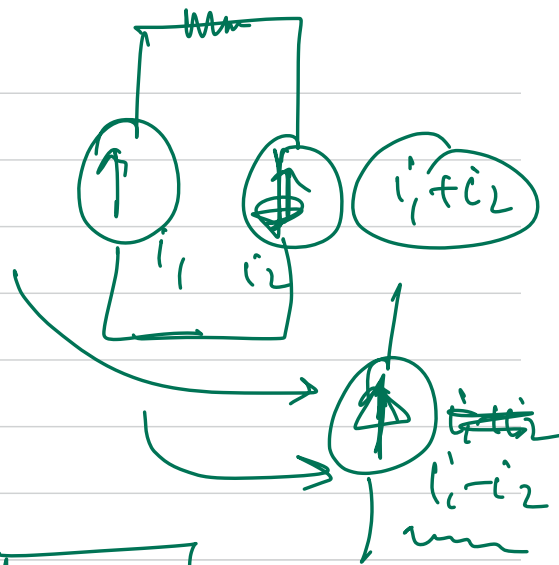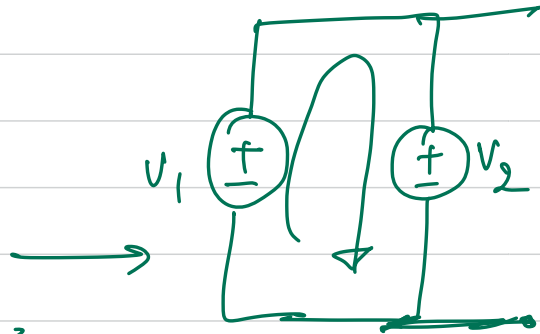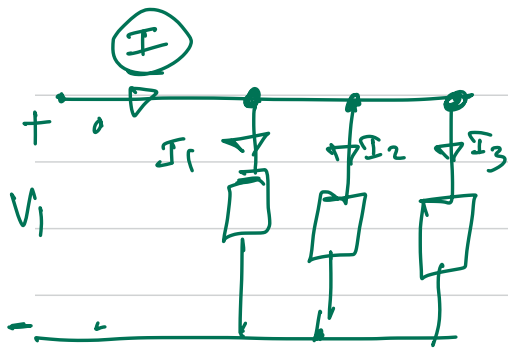

Short circuit

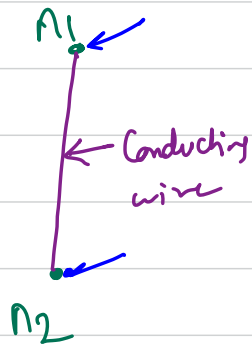


$$V_{n_1} - V_{n_2} = 0$$

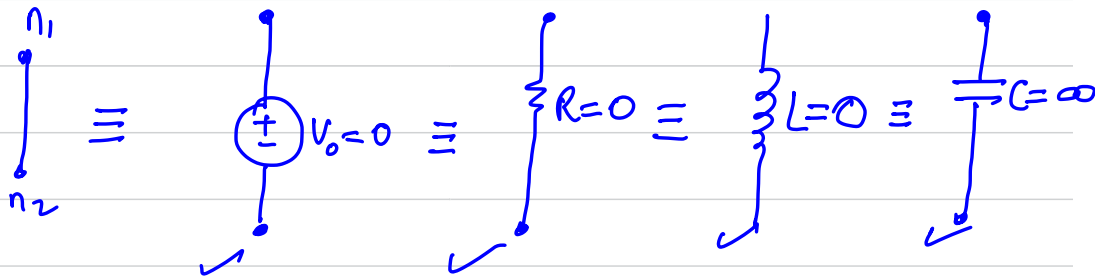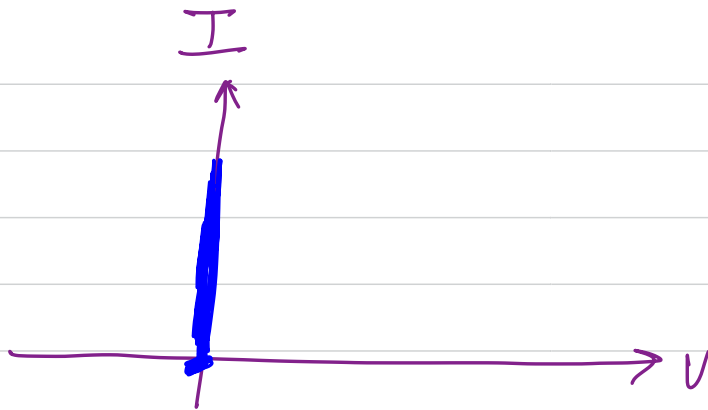


Open circuit


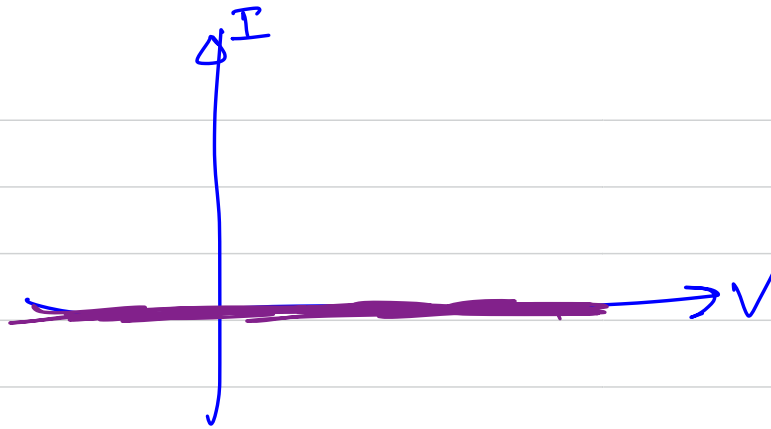
$$\begin{aligned} & \text{Circuit with } I_0 = 0 \equiv \left\{ R = \infty \right\} \equiv \left\{ L = \infty \right\} \equiv \left\{ C = 0 \right\} \end{aligned}$$




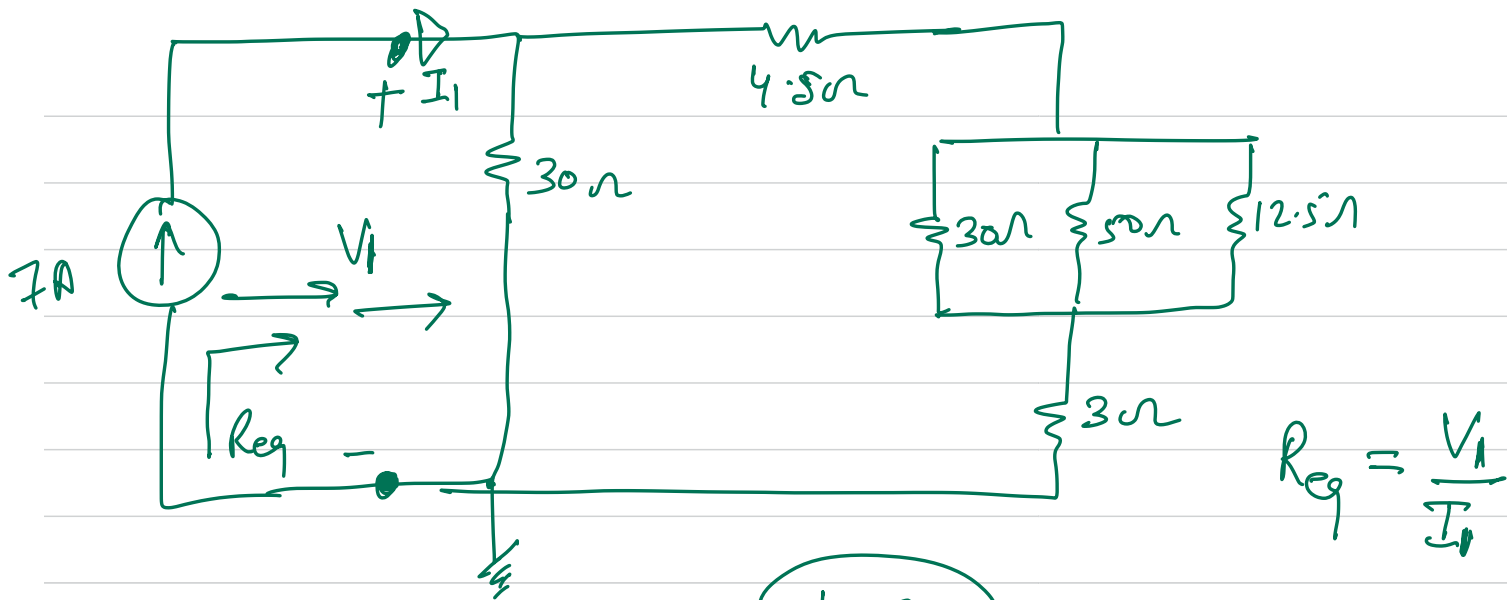


$$R_{eq} = \frac{V_1}{I_1}$$

$$V_1 = 70V$$

$$10\Omega$$

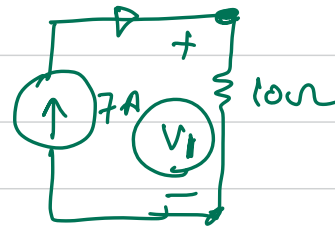



$$10 \times 7 = 70V$$

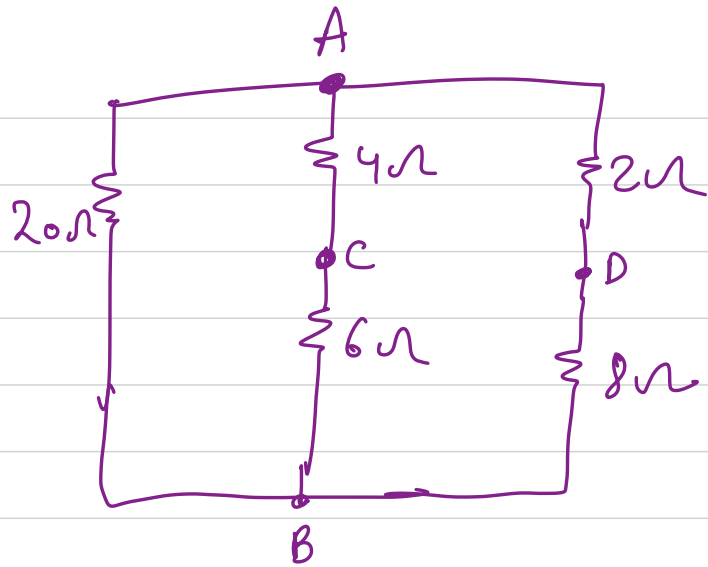


$R_{eq}(A, B) = 4\Omega$

$R_{eq}(A, B)$

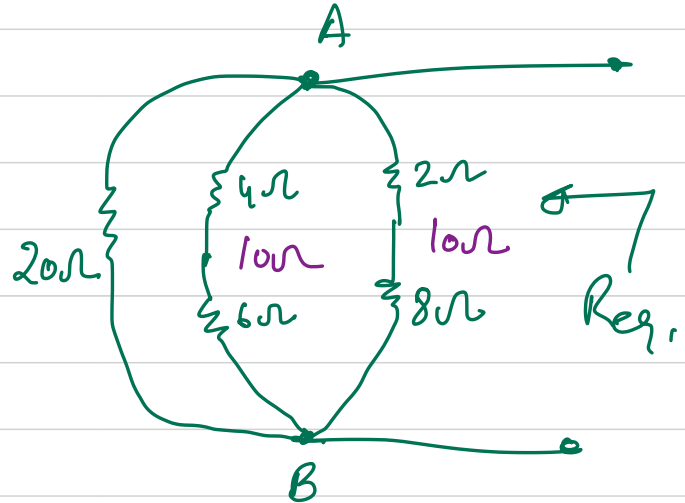


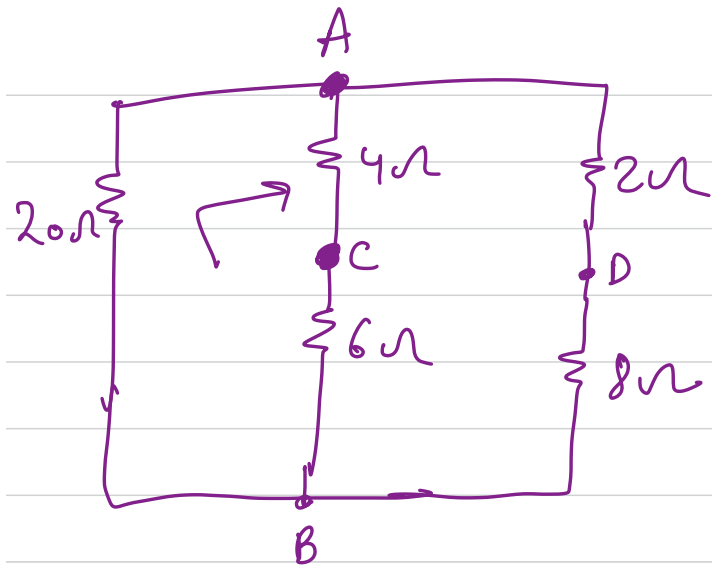


$R_{eq}(A, C)$

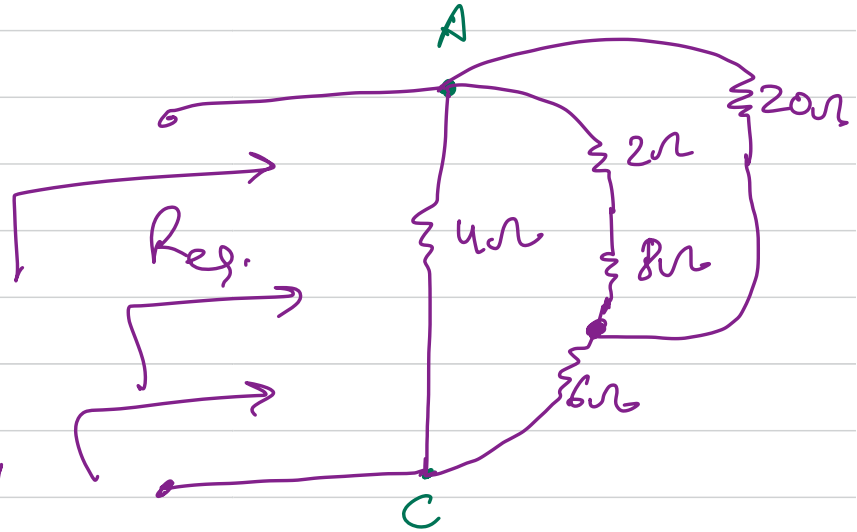

$R_{eq} = 3.04$

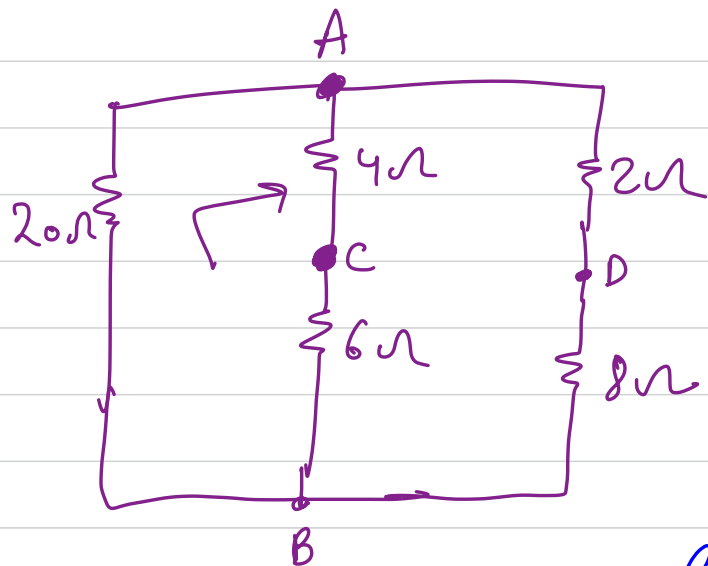

$R_{eq}(CD)$

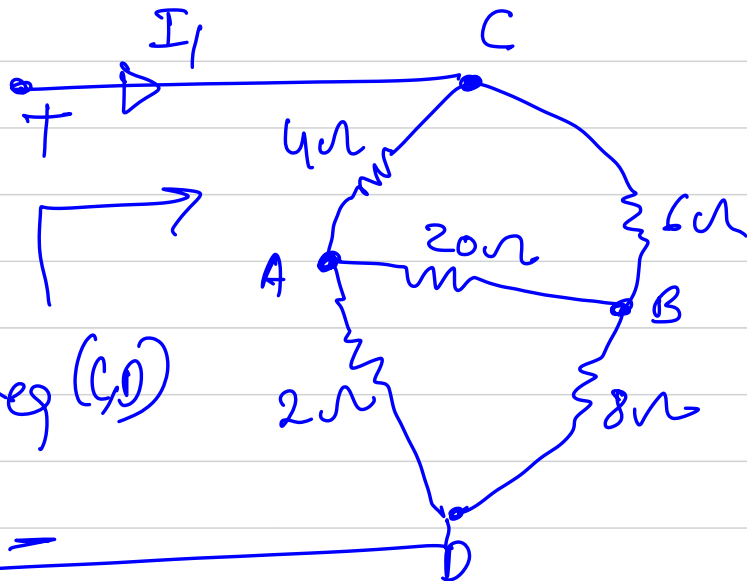

V_1 $R_{eq}(CD)$