

### PRACTICE SHEET 3

1. Using minimum number of 2:1 multiplexers, realize NOT, AND, OR, NAND, NOR, XOR and XNOR (2-input) gates with proper Boolean justification for each.
2. A circuit has eight data inputs ( $A = a_7a_6 \dots a_1a_0$ ), one control input  $P$ , and an 8-bit output ( $Y = y_7y_6 \dots y_1y_0$ ). Design the circuit for the following specifications most economically with respect to the number of gates utilized:
  - (a)  $Y = -A$  using ones' complement representation when  $P = 0$  and  $Y = A$  otherwise
  - (b)  $Y = -A$  using ones' complement representation when  $P = 1$  and  $Y = A$  otherwise

3. Find the values of two-valued variables  $A$ ,  $B$ ,  $C$ , and  $D$  by solving the following set of simultaneous equations:

$$A' + AB = 0$$

$$AB = AC$$

$$AB + AC' + CD = C'D$$

4.
  - (a) Show that  $f(A, B, C) = A'BC + AB' + B'C'$  is a universal operation.
  - (b) Assuming that a constant value 1 is available, show that  $f(A, B) = A'B$  (together with the constant) is a universal operation.

5. The majority function  $M(x, y, z)$  is equal to 1 when two or three of its arguments equal 1, that is,

$$M(x, y, z) = xy + xz + yz = (x + y)(x + z)(y + z)$$

Show that:

- (a) Show that  $M(a, b, M(c, d, e)) = M(M(a, b, c), d, M(a, b, e))$ .
- (b) Show that  $M(x, y, z)$ , the complementation operation, and the constant 0 form a functionally complete set of operations.
- (c) Find the simplest switching expression  $f(A, B, C, D)$  corresponding to the network of Fig. 1.

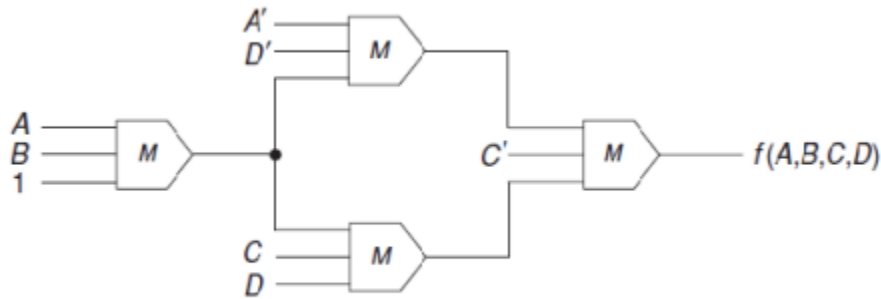


Figure 1: Majority circuit

6. You are presented with a set of requirements under which an insurance policy will be issued. The applicant must be

1. a married female 25 years old or over, or
  2. a female under 25, or
  3. a married male under 25 who has not been involved in a car accident,
- or
4. a married male who has been involved in a car accident, or
  5. a married male 25 years or over who has not been involved in a car accident.

Variables  $w$ ,  $x$ ,  $y$ , and  $z$  assume truth value 1 in the following cases:

$w = 1$  if the applicant has been involved in a car accident;

$x = 1$  if the applicant is married;

$y = 1$  if the applicant is a male;

$z = 1$  if the applicant is under 25.

(a) Find an algebraic expression that assumes the value 1 whenever the policy should be issued.

(b) Simplify algebraically the above expression and suggest a simpler set of requirements.

7. Prove that for every Boolean algebra:

(a)  $a + a'b = a + b$

(b) if  $a + b = a + c$  and  $a' + b = a' + c$ , then  $b = c$

(c) if  $a + b = a + c$  and  $ab = ac$ , then  $b = c$

8. Given the function  $T(w, x, y, z) = \Sigma m(1, 3, 4, 5, 7, 8, 9, 11, 14, 15)$ ,
- use the map to obtain the set of all prime implicants and indicate specifically the essential ones
  - find three distinct minimal expressions for  $T$
  - find the complement  $T$  directly from the map
9. A newly proposed 3-input gate  $T$  has logical properties that is defined in Fig. 2.
- Prove that if the logic value 1 is given, then any switching function can be realized using only the newly proposed  $T$  gates, that is,  $T$  gates along with the logic value 1 are functionally complete.
  - Realize, by means of two  $T$  gates, the function  $f(w, x, y, z) = \Sigma m(0, 1, 2, 4, 7, 8, 9, 10, 12, 15)$ .

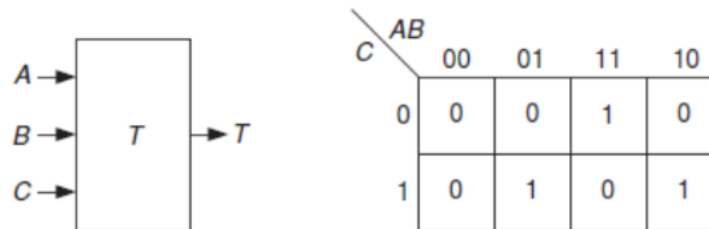


Figure 2: Gate  $T$

10. A switching circuit has two control inputs ( $C1$  and  $C2$ ), two data inputs ( $X1$  and  $X2$ ), and one output ( $Z$ ). The circuit performs one of the logic operations AND, OR, EQU (equivalence), or XOR (exclusive OR) on the two data inputs. The function performed depends on the control inputs:

$C1$	$C2$	Function performed by the circuit
0	0	OR
0	1	XOR
1	0	AND
1	1	EQU

- Derive a truth table for  $Z$ .

(b) Use a Karnaugh map to find a minimum AND-OR gate circuit to realize Z.

11. A switching circuit has four inputs as shown in Fig. 3. A and B represent the higher and lower order bits of a binary number N1. C and D represent higher and lower order bits of a binary number N2. The output is to be 1 only if the product  $N1 \times N2$  is less than or equal to 2.

(a) Find the minterm expansion for F and the minimal SOP form.

(b) Find the maxterm expansion for F and the minimal POS form.

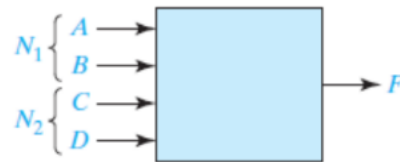


Figure 3: Switching circuit

12. Using only 2-input logic gates, design a 6-bit combined ones' complementer and two's complementer circuit most optimally, such that when the control input  $P = 1$ , circuit performs a ones' complement operation, and two's complement otherwise.

13. (a) Using only 2-input logic gates, design most optimally, a 5-bit circuit that computes  $Y = X + 2$ .

(b) How will you re-design this circuit most optimally, by making minimal changes to the solution proposed in 13(a), to build a controlled incrementer logic that computes  $Y = X + 2$  if  $P = 0$  and  $Y = X + 1$  if  $P = 1$ ?

14. Using only 2-input logic gates, design a 4-bit controlled decrementer circuit which accepts a 4-bit number  $A$  and outputs a 4-bit number  $Y$  and has an additional control bit  $P$ . If  $P = 0$ ,  $Y = A - 1$ ; otherwise  $Y = A$ .