
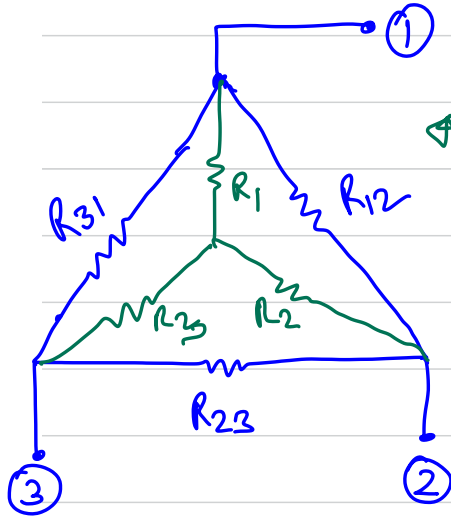


Lecture 6

Star-Delta transformation

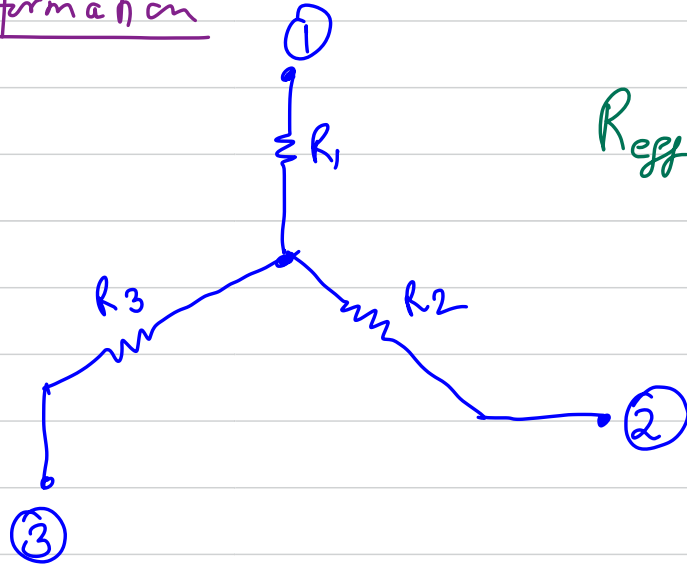

$R_{eff(1,2)}$



$R_{eff(1,2)}$

$$R_1 \parallel (R_2 + R_3) = (R_1 + R_2) \quad R_{\text{eff}(1,2)}$$

$$R_2 \parallel (R_1 + R_3) = (R_2 + R_3) \quad R_{\text{eff}(2,3)}$$

$$R_3 \parallel (R_1 + R_2) = (R_1 + R_3) \quad R_{\text{eff}(1,3)}$$

$$R_1 = \frac{R_2 R_3}{R_2 + R_3 + R_1}$$

$$R_2 = \frac{R_1 R_3}{R_1 + R_3 + R_2}$$

$$R_3 = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{31} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

"Controlled Sources"




→ Voltage Controlled voltage source (VCVS) e


→ Voltage Controlled Current source (VCCS) g

→ Current Controlled voltage source (CCVS) h

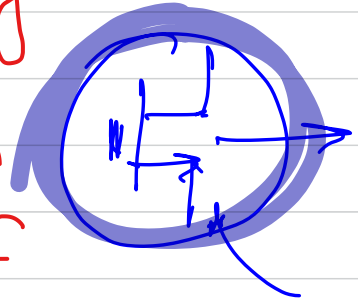→ Current Controlled Current source (CCCS) f




VCVS

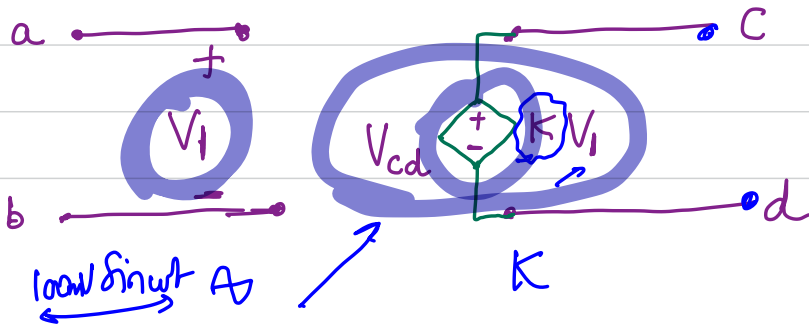


$$V_{cd} = K V_{ab}$$


VCCS

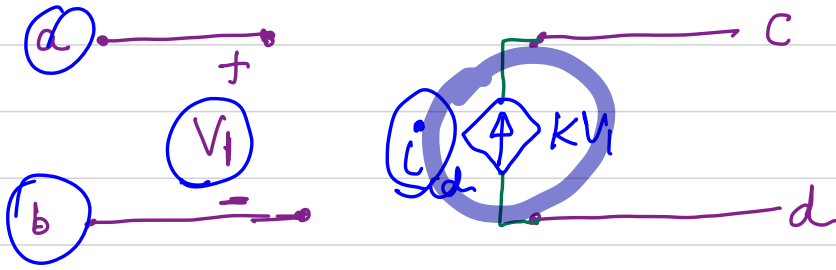


$$i_c = KV_{ab}$$

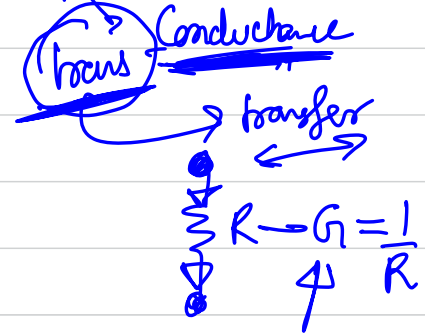


CC VS

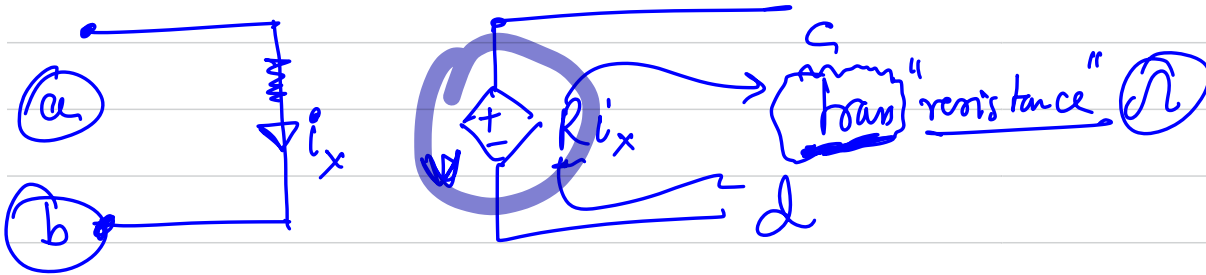


CC CS

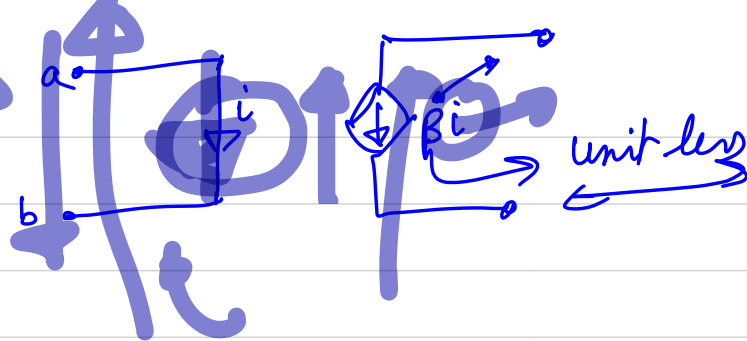

Q

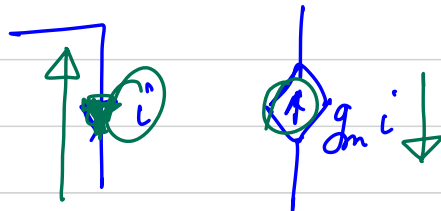


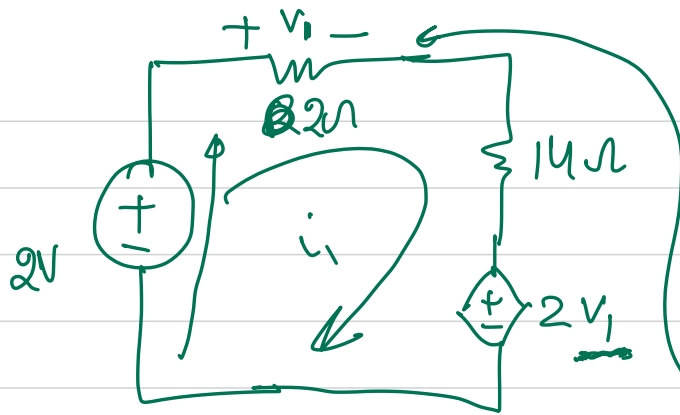

$$2 - 2xi_1 - 14i_1 - 2V_1 = 0$$

$$V_1 = 2i_1$$

$$i_1 = ? \quad 0.1 \text{ Amp}$$

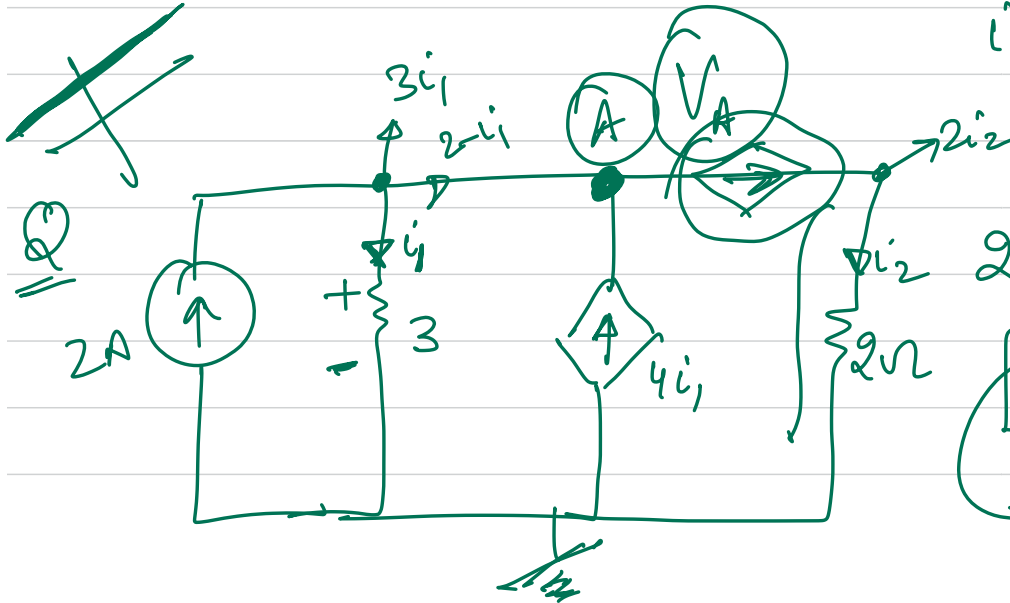

$$2A + 4i_1 = i_1 + i_2$$


$$2 + 3i_1 = i_2$$

$$3i_1 = 2i_2 \quad i_2 = -2A$$

$$i_1 = -4/3$$

{ Nodal Analysis } \rightarrow "KCL"

Circuits resistors & current source.

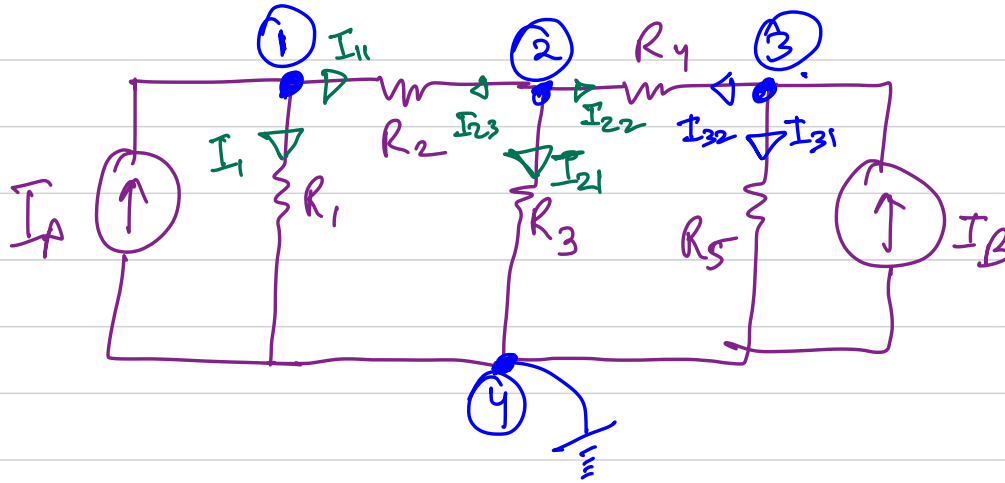

$$I_B = \underline{I_{31}} + I_{32}$$

$$V_3 G_5 + (V_3 - V_2) G_4 = I_B$$

$$+ V_1 \cdot 0 - V_2 G_4 + V_3 (G_5 + G_4) = I_B$$

$$I_1 + I_{11} = I_A$$

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} = I_A \rightarrow V_1 (G_1 + G_2) - V_2 G_2 = I_A \rightarrow \textcircled{1}$$

$$I_{21} + I_{22} + I_{23} = 0 \quad V_2 G_3 + (V_2 - V_3) G_4 + (V_2 - V_1) G_2 = 0$$

$$-V_1 G_2 + V_2 (G_3 + G_4 + G_2) - V_3 G_4 = 0 \quad \textcircled{2}$$


$$V_1 (G_1 + G_2) - V_2 G_2 + V_3 \cdot 0 = I_A \longrightarrow \text{node 1}$$

$$-V_1 (G_2) + V_2 (G_2 + G_3 + G_4) - V_3 G_4 = 0 \longrightarrow \text{node 2}$$

$$V_1 \cdot 0 - V_2 G_4 + V_3 (G_5 + G_4) = I_B \longrightarrow \text{node 3.}$$

$$\begin{bmatrix} G_1 + G_2 & -G_2 & 0 \\ -G_2 & G_2 + G_3 + G_4 & -G_4 \\ 0 & -G_4 & G_5 + G_4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_A \\ 0 \\ I_B \end{bmatrix}$$

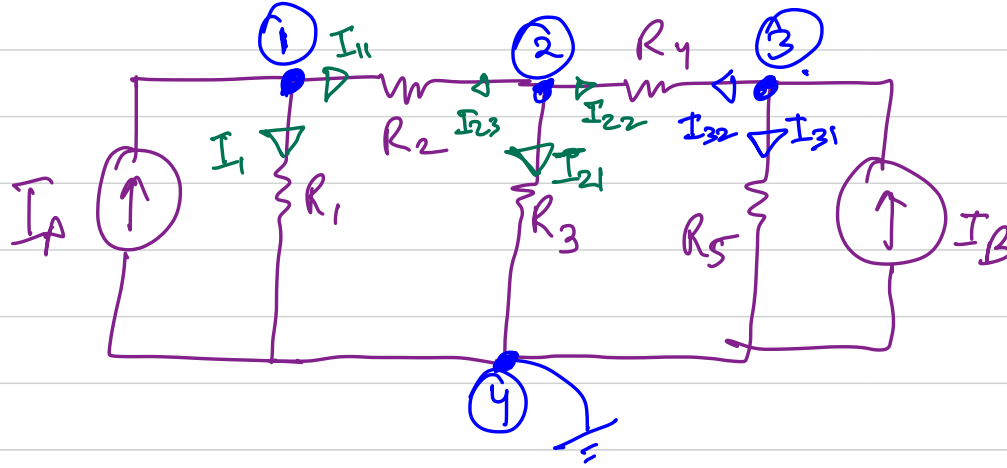$\xleftarrow{\text{Conductance Matrix}}$
 $\xleftarrow{\text{Unknown Variable}}$
 $\xleftarrow{\text{"Current source" / voltage source}}$



$$GV = I$$

$$V = G^{-1} I$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \\ 3 \end{bmatrix}$$