

Practice Sheet 4

1. Find the minimal sum-of-products and minimal product-of-sums expressions for:

$$f(w, x, y, z) = \Pi(1, 4, 5, 6, 11, 12, 13, 14, 15)$$

Is your answer unique?

2. A binary-coded-decimal (BCD) message appears in four input lines of a switching circuit. Design an AND, OR, NOT gate network that produces an output value 1 whenever the input combination is 0, 2, 3, 5 or 8.
3. Each of the following functions actually represents a set of four functions, corresponding to the possible assignments of the don't-care terms.

$$f_1(w, x, y, z) = \Sigma m(1, 3, 4, 5, 9, 10, 11) + \Sigma d(6, 8)$$

$$f_2(w, x, y, z) = \Sigma m(0, 2, 4, 7, 8, 15) + \Sigma d(9, 12)$$

(a) Find $f_3 = f_1 \cdot f_2$ using Σm and Σd notation, along with SOP and POS function. How many functions does f_3 represent?


(b) Find $f_4 = f_1 + f_2$ using Σm and Σd notation, along with SOP and POS function. How many functions does f_4 represent?

(Hint: Just for expressing f_3 and f_4 using Σm and Σd notation, you need not minimize f_1 and f_2 using Karnaugh maps).

4. Let $f = \Sigma m(5, 6, 13)$, and $f_1 = \Sigma m(0, 1, 2, 3, 5, 6, 8, 9, 10, 11, 13)$.

Find f_2 such that $f = f_1 f_2$ both using SOP and POS. Is f_2 unique? If not, indicate all possibilities; (you may state it in words, and not necessarily derive functions for all possibilities if at all multiple possibilities exist).

 5. From the circuit given below, determine the functions f_2 and f_3 if $f_1 = xz' + x'z$, and the overall transmission function is $f(w, x, y, z) = \sum m(0, 4, 9, 10, 11, 12)$
- (Hint: You need not minimize f using Karnaugh maps to determine f_2 and f_3)



6. Find the minimum sum of products and the minimum product of sums for each function:
- $f(a, b, c, d) = \prod m(0, 1, 6, 8, 11, 12) \cdot \prod d(3, 7, 14, 15)$
 - $f(a, b, c, d) = \sum m(1, 3, 4, 11) + \sum d(2, 7, 8, 12, 14, 15)$
 - $f(a, b, c, d, e) = \sum m(0, 1, 2, 6, 7, 9, 10, 15, 16, 18, 20, 21, 27, 30) + \sum m(3, 4, 11, 12, 19)$
 - $f(a, b, c, d, e) = \prod m(0, 3, 6, 9, 11, 19, 20, 24, 25, 26, 27, 28, 29, 30) \cdot \prod d(1, 2, 12, 13)$
7. A combinational network with four inputs A, B, C, and D, three intermediate outputs Q, P, and R, and final two outputs T1 and T2 is shown in Fig. 2.
- Assuming that G_1 and G_2 are both AND gates, show the map for the smallest function P_{min} (i.e., with the minimum number of minterms) that makes it possible to produce T1 and T2.
 - Show the maps for Q and R that correspond to the above P_{min} . Indicate explicitly the don't-care positions.
 - Assuming that G_1 and G_2 are both OR gates, find the largest P_{max} and show the corresponding maps for Q and R.

 


Figure 2: Combinational network

8. You are supplied with just one NOT gate and an unlimited amount of AND and OR gates and are required to design a circuit that realizes the expression

$$T(w, x, y, z) = w'x + x'y + xz'$$

Only unprimed variables are available as inputs. (Hint: You may find the map of T helpful.)

9. A certain four-input gate, called a LEMON gate, realizes the switching function $\text{LEMON}(A,B,C,D) = BC(A + D)$. Assume that the input variables are available in both primed and unprimed form.

(a) Show a realization of the function $f(w, x, y, z) = \sum m(0, 1, 6, 9, 10, 11, 14, 15)$ with only three LEMON gates and one OR gate.

(b) Can all switching functions be realized with LEMON and OR logic?

(Hint: Draw the map for LEMON and utilize possible “patches” (coverings of the minterms of f with the LEMON function) on the map of f.)

10. A logic module A, shown in Fig. 3, operates as follows: output $y_i = 1$ if and only if i inputs out of x_0, x_1, x_2 are equal to 1. Design unit B in such a way that the overall logic function of unit C will be to produce an output $z_i = 1$ if and only if i inputs out of x_0, x_1, x_2, x_3 are equal to 1.

 


Figure 3: Logic modules

11. (a) Write the complete truth table of a 2:1 multiplexer. Re-write the truth table using don't-care combinations at the inputs to reduce the number of rows of the truth table.
 (b) Using don't-care combinations at the inputs, write the truth table of a 4:1 multiplexer.
 (c) Draw the gate level implementation of a 4:1 multiplexer using NAND gates only.
12. (a) Using 2-input gates ONLY, design a 4-bit controlled incrementer /decrementer circuit, which performs increment operation when a control input $P = 0$, and performs decrement operation otherwise.

- (b) Using the 4-bit controlled incrementer / decrementer circuit as a sub-circuit, design a 16-bit controlled incrementer / decrementer.
13. (a) Using 2-input gates ONLY, design a 4-bit controlled 2's complementer circuit, which performs 2's complementation when a control input $P = 1$, and leaves the input unchanged otherwise.
- (b) Using the 4-bit controlled 2's complementer circuit as a sub-circuit, design a 16-bit controlled 2's complementer circuit.
14. Design a 4-bit leading one detector. The detector circuit accepts a 4-bit input and generates a 4-bit output string with a single logic 1 exactly at that position where the first 1 is encountered, starting from the MSB side of the input. If the input comprises all zero bits, the output is identical to the input. Do not use gates having a fan-in of more than two.
15. Using a single 2:1 multiplexer and two 2-input XOR gates, construct a full adder cell. (Hint: You may use the concept of carry propagate driving the select line of the multiplexer.)